
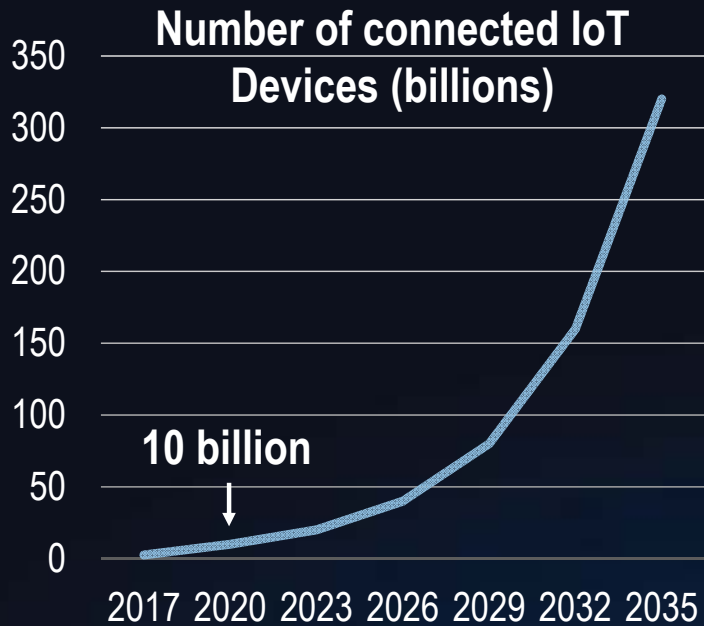


Energy Harvesting and Self-Powered Sensing for Next-Generation "Unaware-ables" and IoT

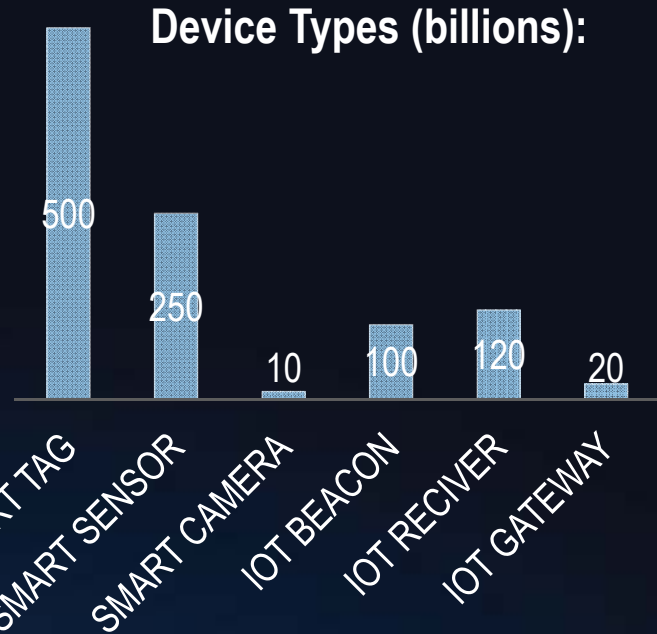Patrick Mercier
University of California, San Diego




Cumulative total:
~1 trillion IoT
 devices by 2035



CHALLENGE: How to power 1 trillion devices?



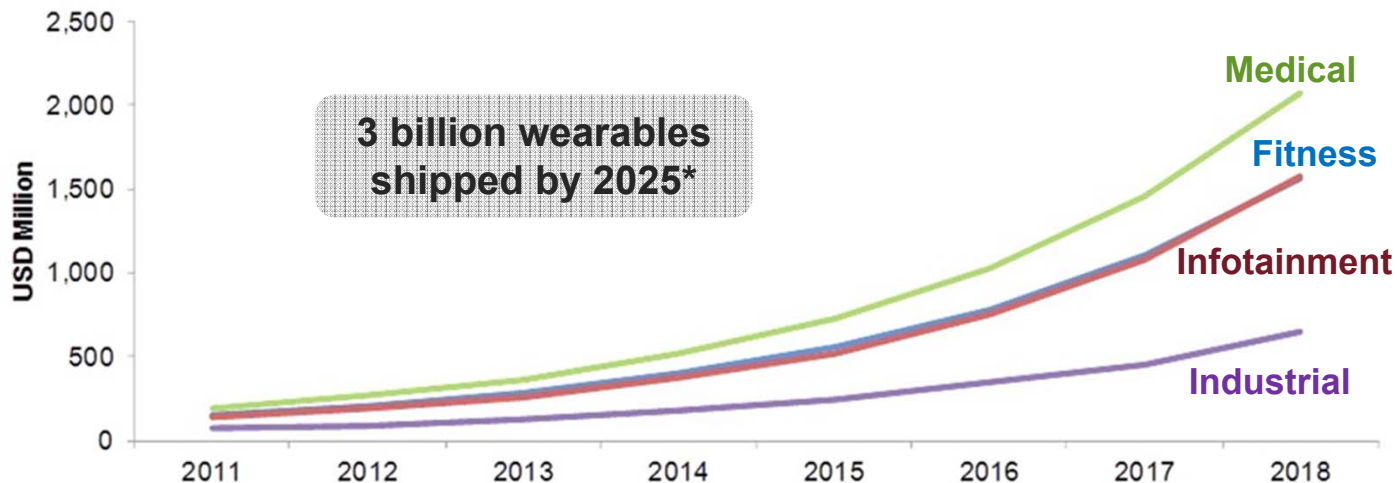Wearables: an exciting high-growth market



*IDTechEx 2015 Report

Source: Transparency Market Research

Why aren't we there now?



Size & Usability:

Need to develop sensors that are small & seamlessly integrated into daily life

Battery Life:

Need ultra-low-power and/or energy harvesting to minimize re-charging


Utility:

Need to develop sensors that are actually useful

Mission:

Address these issues through innovative transdisciplinary research

Wearables Roadmap

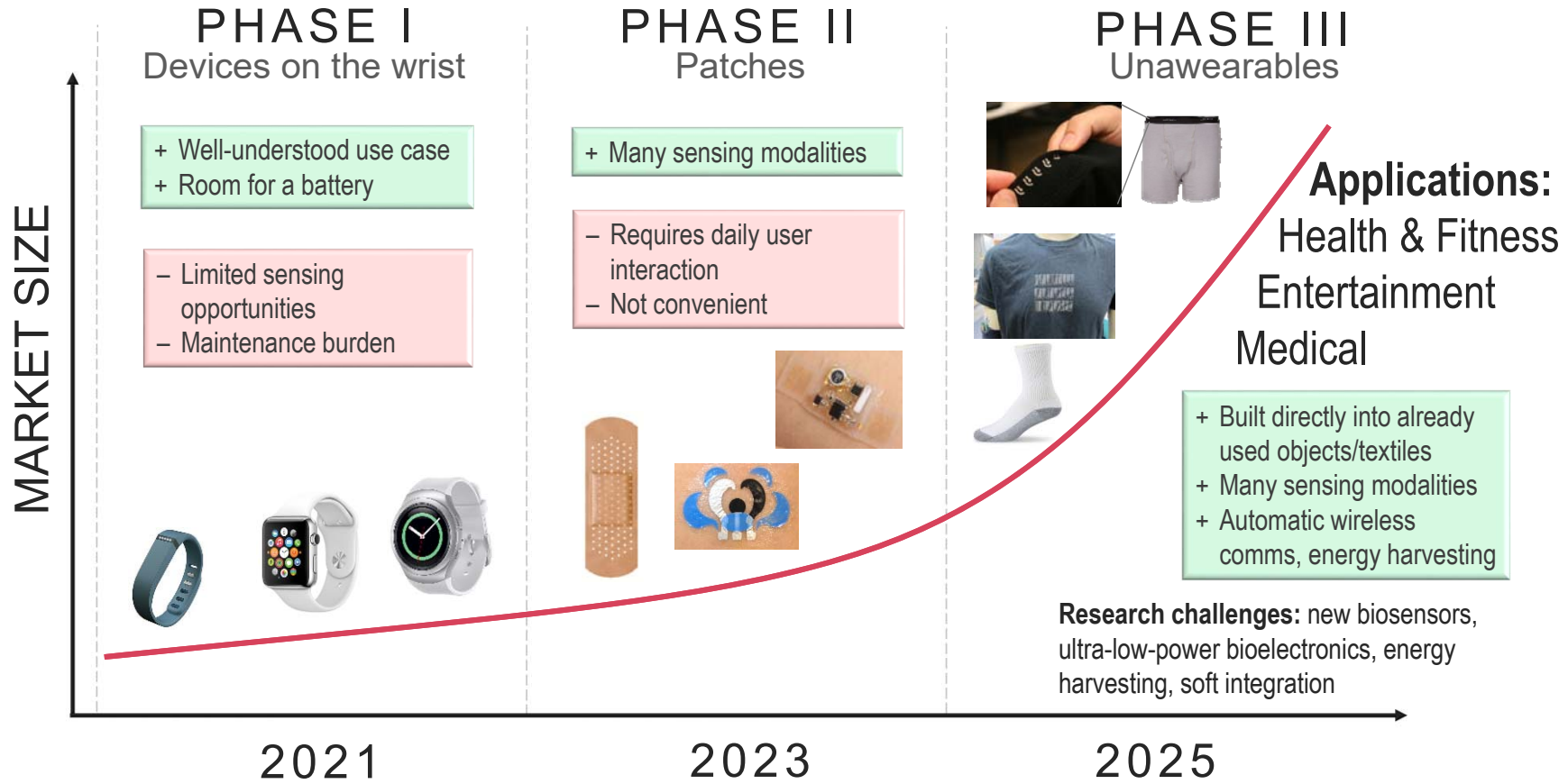

Why aren't we there now?



Size & Usability:

Need to develop sensors that are small & seamlessly integrated into daily life

Battery Life:

Need ultra-low-power and/or energy harvesting to minimize re-charging

Utility:

Need to develop sensors that are actually useful

Mission:

Address these issues through innovative transdisciplinary research



Pushing the frontier on new wearable sensing technologies

Non-invasive glucose and alcohol sensing

Sweat **ISF**


Dual Iontophoresis

J. Kim et al., Advanced Science'18

Hybrid physiochemical & electrophysiological sensing




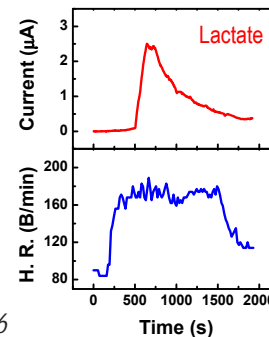S. Imani et al., Nature Communications'16



First demonstration of real-time ECG+lactate recording

Real-time saliva sensors

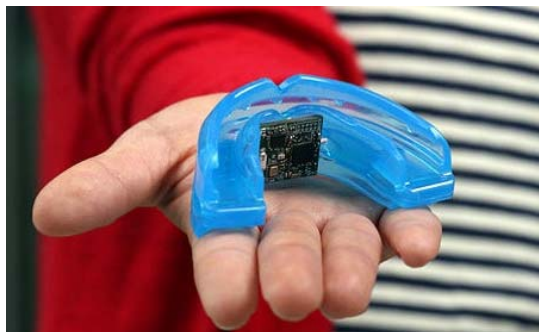


Physiochemical analysis in saliva

Startup company:

TRAQ

J. Kim et al., Biosensors & Bioelectronics'15


Bio-energy harvesting

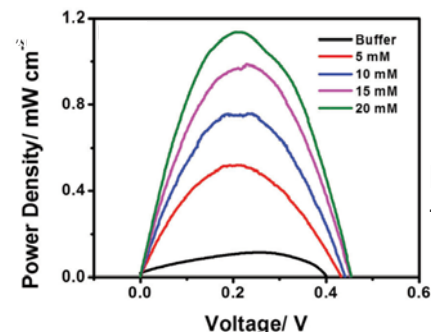


1mW/cm² harvested from sweat

A.J. Bandodkhar et al., EES'17

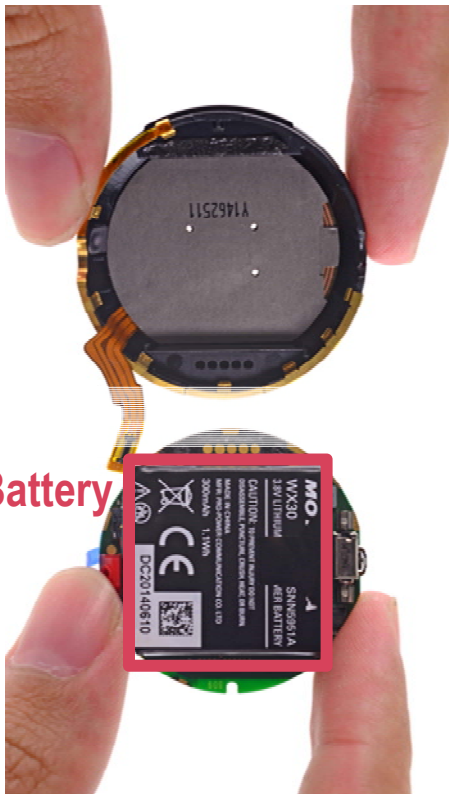Major limiter in IoT devices: battery size / battery life




Battery

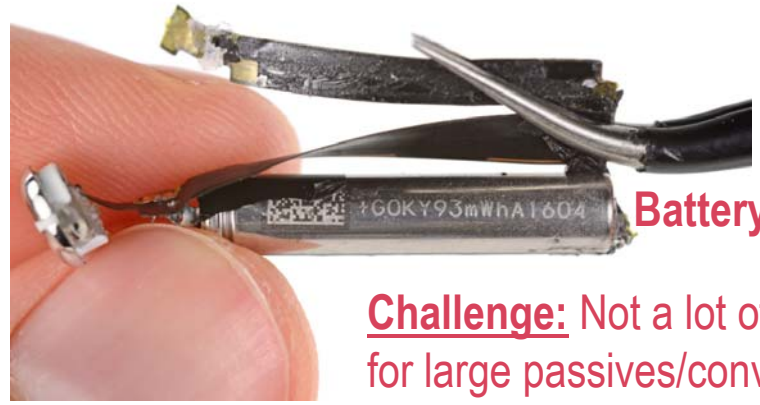


Challenge: Not a lot of room for large passives/converters

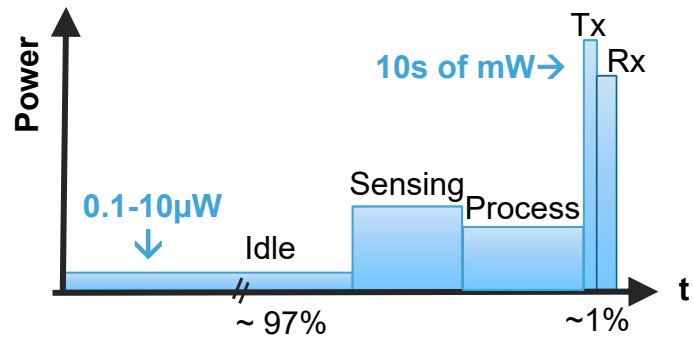Challenge: Require high efficiency over 1,000,000x dynamic range




Research goal:
 Simultaneously increase efficiency and power density over a wide dynamic range

Conventional

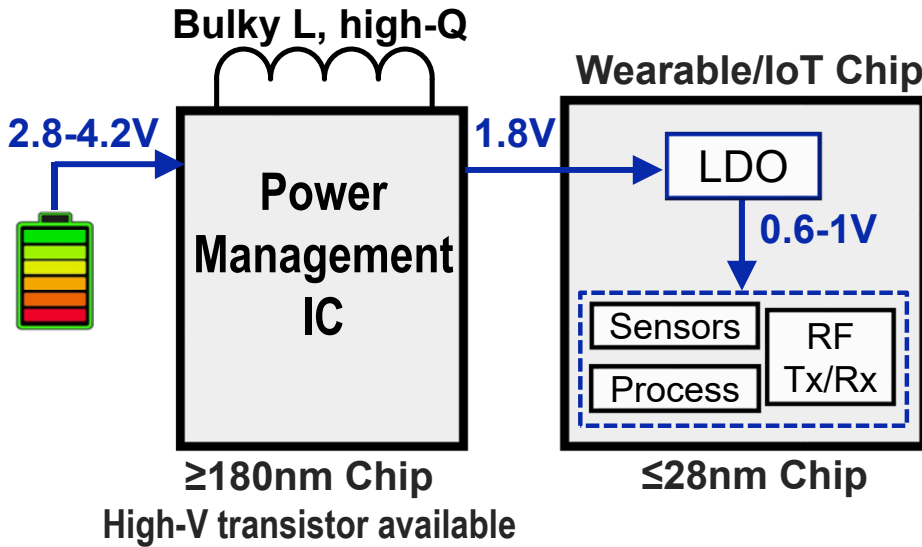

Goal

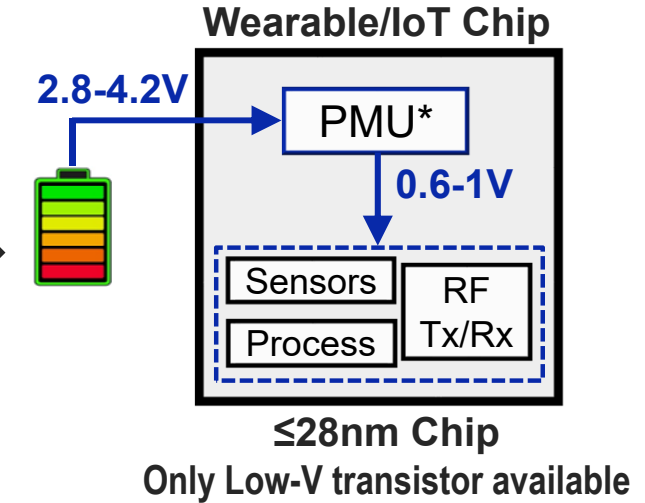

PMU*: Power Management Unit with or without off-chip inductor



Li-ion Fully-Integrated PMU Challenges in 28nm FDSOI

Scaled-CMOS Challenges

Only Low-V transistors available

Transistors stacking required

- High switching & conduction losses
- Complex power-hungry drivers
- Many level shifters

Poor efficiency

Only Low-V capacitors available

Capacitors stacking required


Large area

Low power density

Poor quality on-chip passives


- Large ESR, parasitic cap
- Low density

Poor efficiency
Low power density

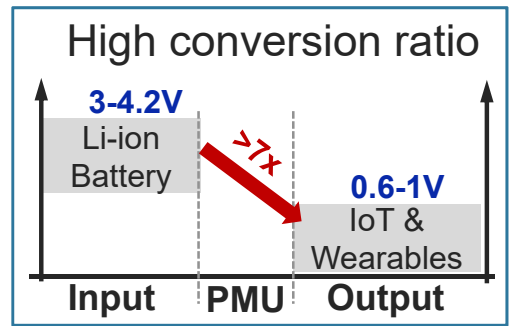




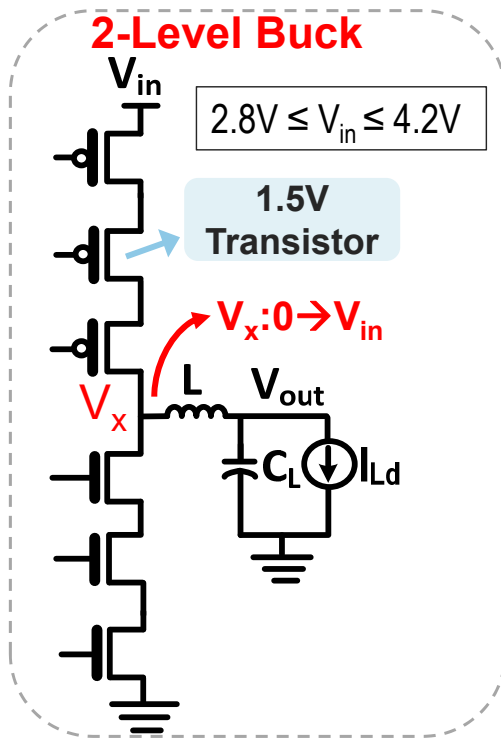Towards Fully-Integrated Li-ion PMU in Scaled CMOS



Small on-chip L, large ESR

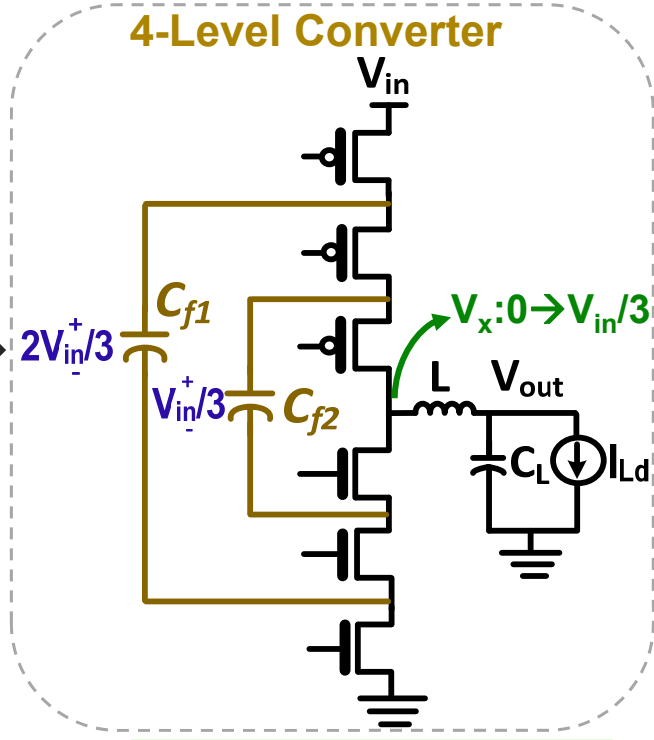
- High Switching & conduction losses
- Poor efficiency



Reduced swing at Vx

F_{sw} reduced by $> 23x$
& efficiency by up to 33%

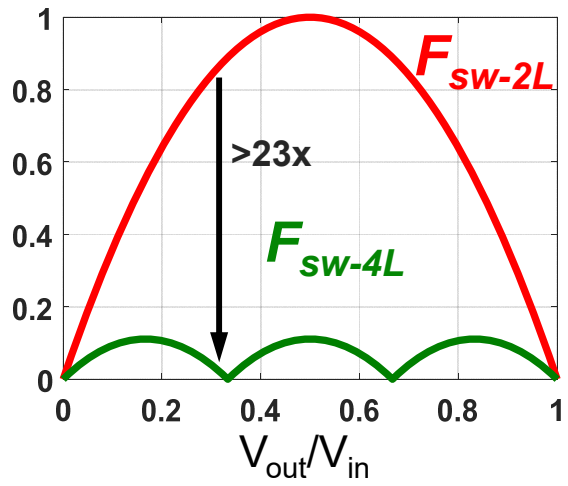
DCM-operated
Constant I_{pk}
Normalized Switching Frequency



$$\frac{F_{sw-4L}}{F_{sw-2L}} = \frac{1/3 - V_{out}/V_{in}}{1 - V_{out}/V_{in}}$$


Conventional 4-Level Converter Area Penalty

Conventional 4-Level

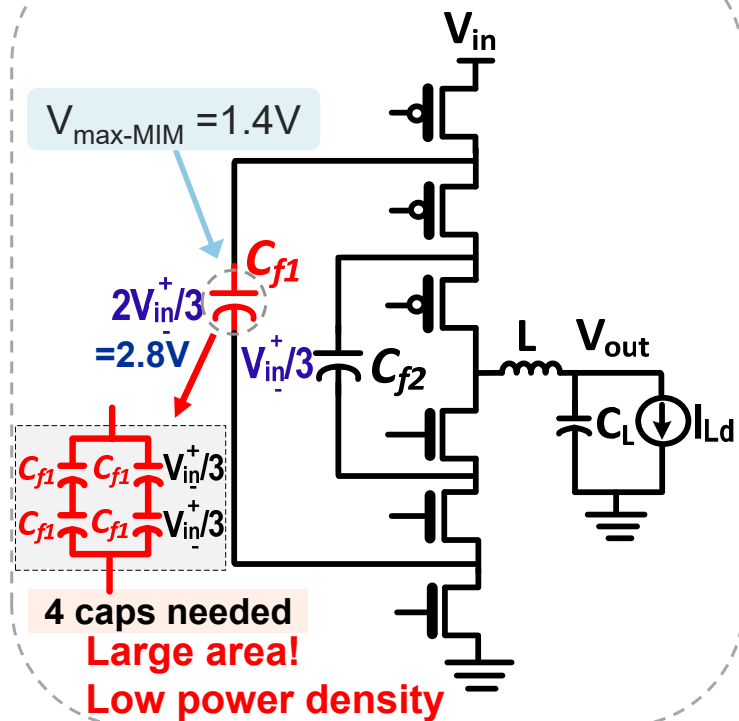


Reducing cap area by 4x

Proposed Modified 4-Level


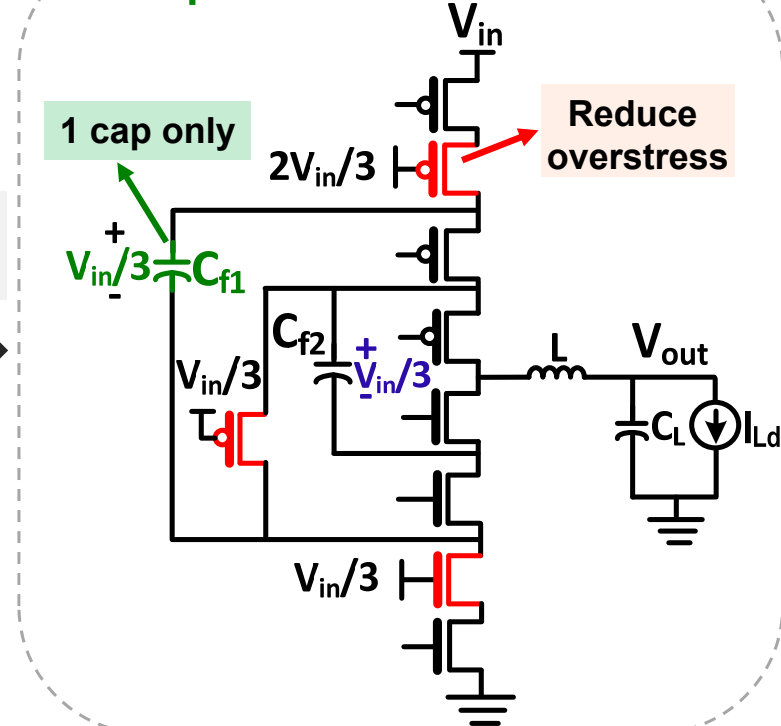


Changing the switching states of flying caps reduces the cap voltage stress



Driver Architecture

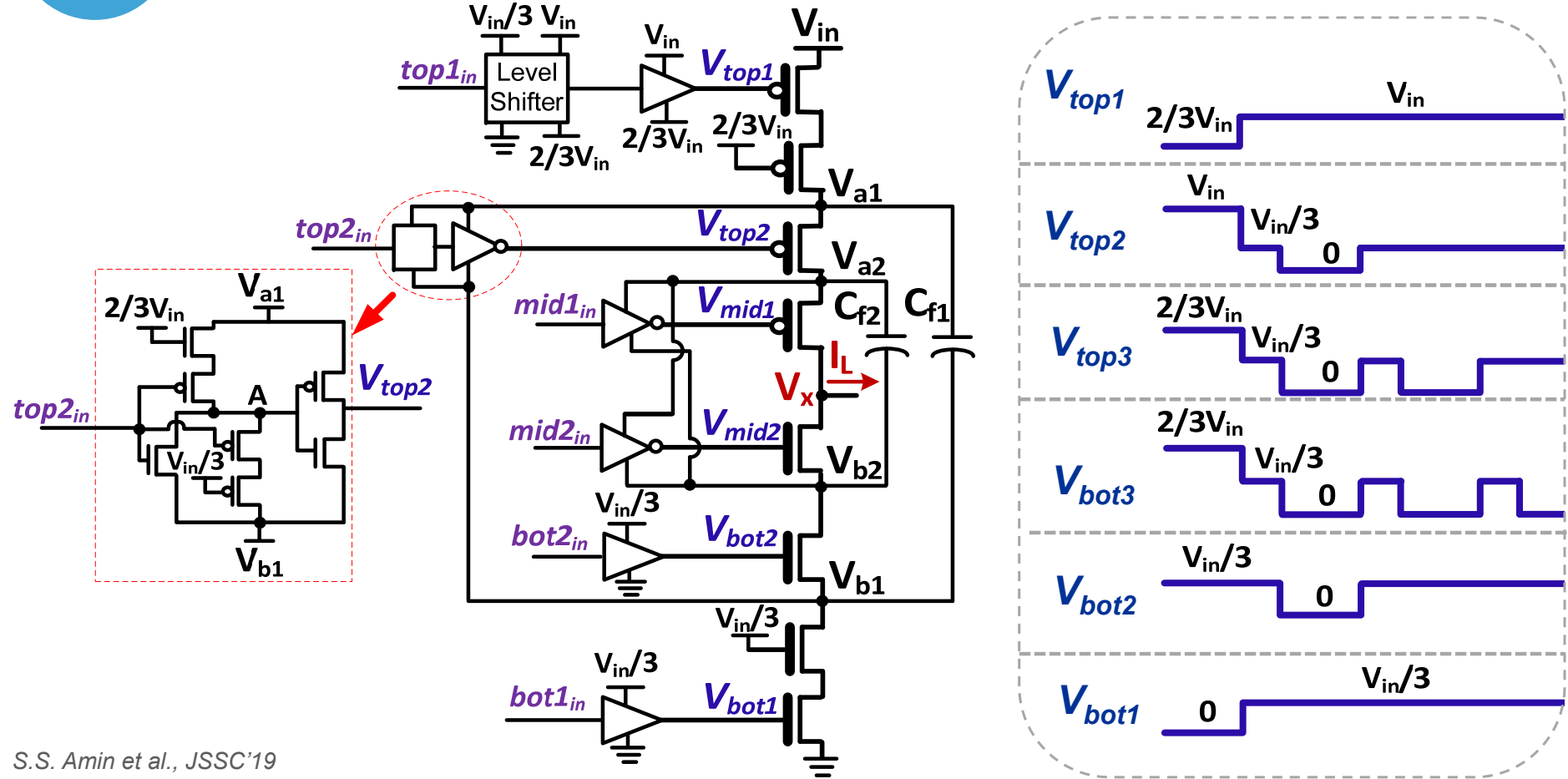


Measurement Results

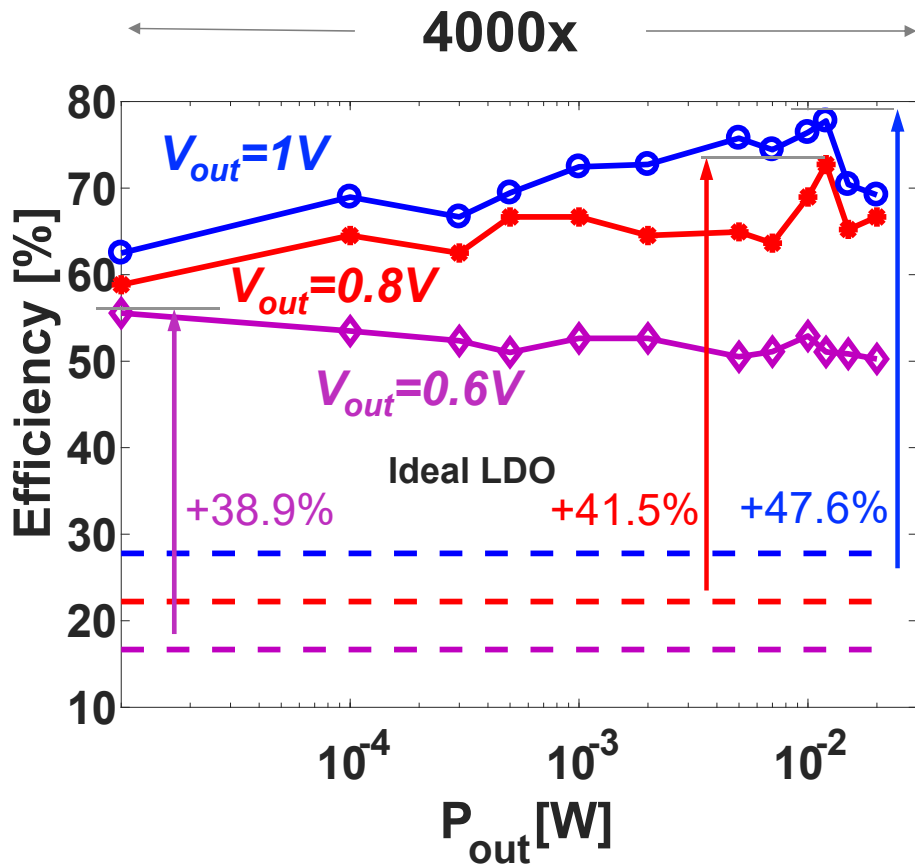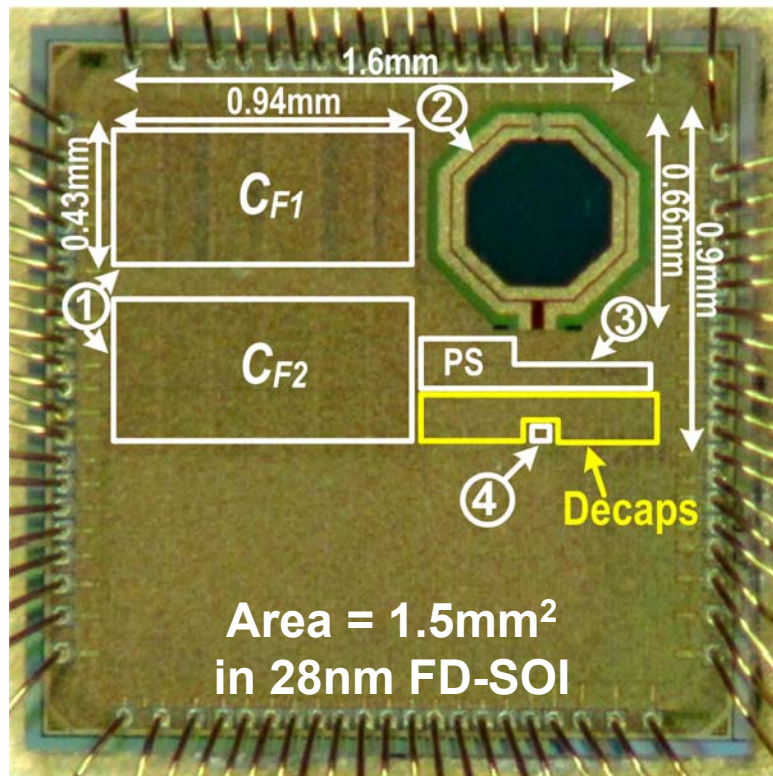

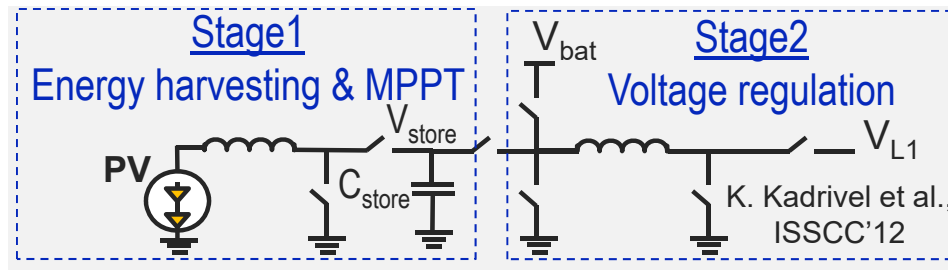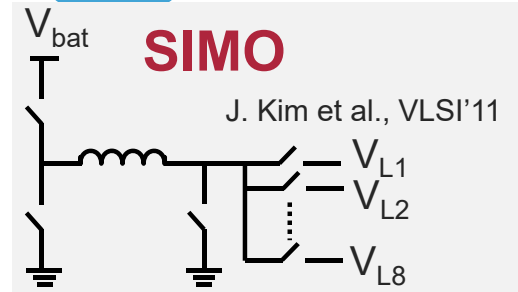
Towards Small Form-Factor Single-Inductor Converters



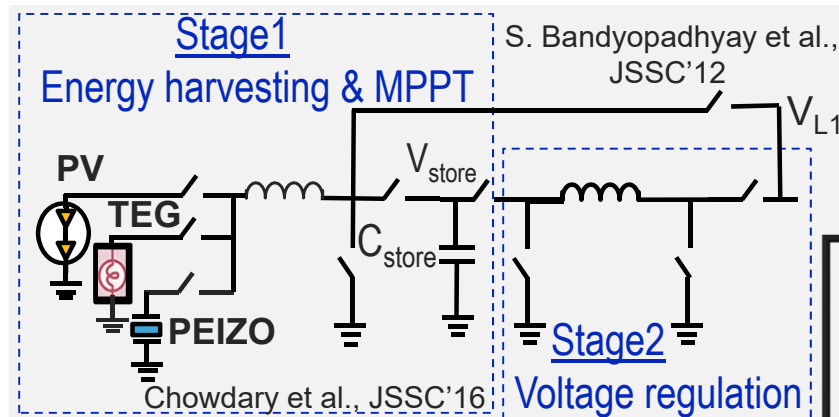
- Single input
- Single output
- Cascaded losses



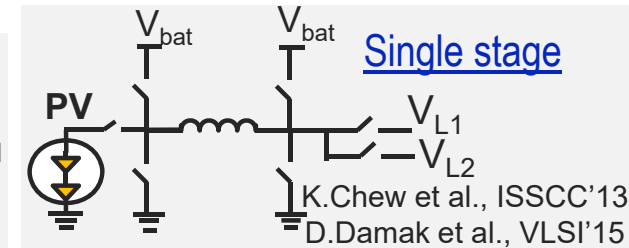- + Multiple inputs
- Cascaded losses
- Single output



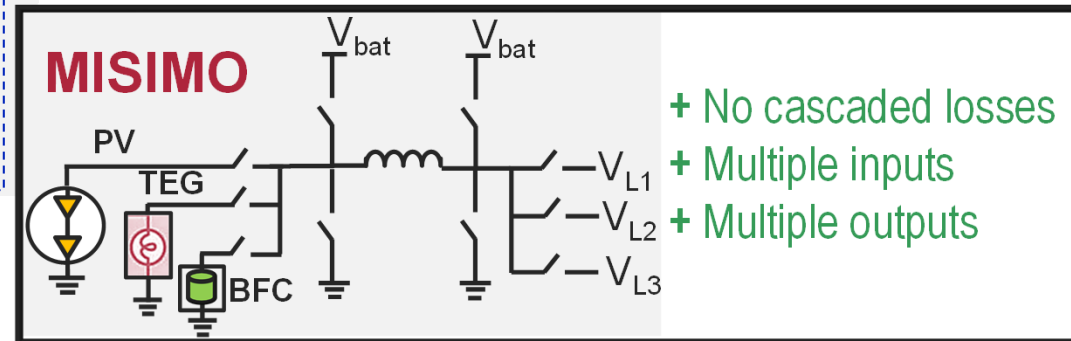
- + No cascaded losses
- + Multiple outputs
- Single input





- + No cascaded losses
- + Multiple inputs
- + Multiple outputs



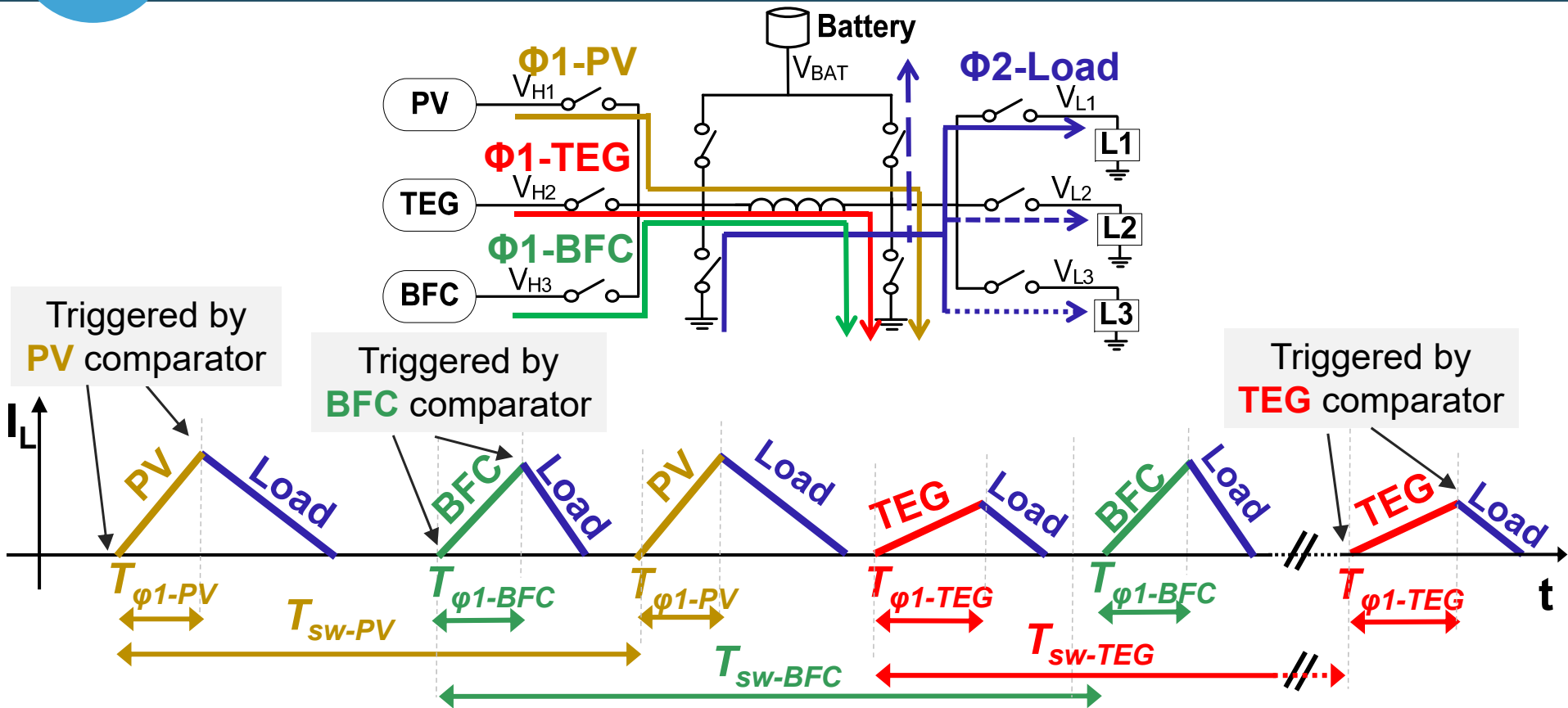
Time-Shared Inductor for Multi-Input Harvesting



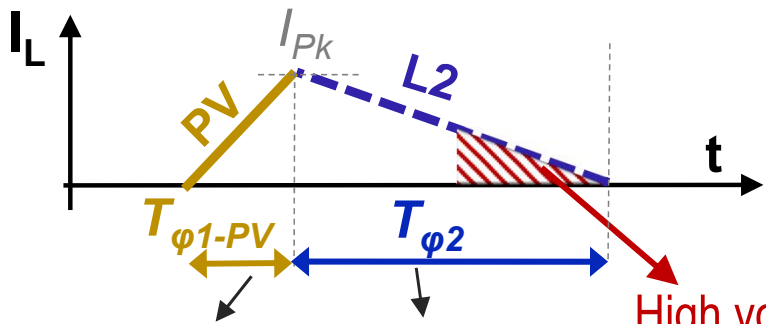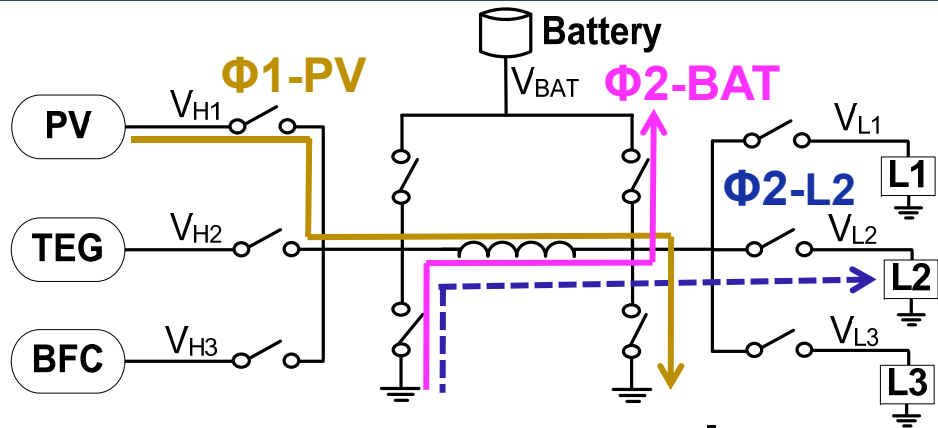Challenge: decoupling MPPT and Load Regulation



Proposed

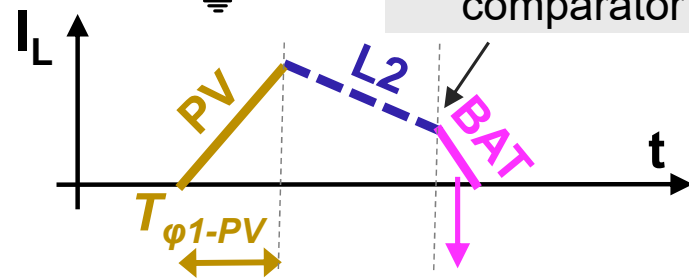

Triggered by load comparator

High voltage ripple
Degraded load regulation

Extra charge recycled to battery
MPPT & load regulation decoupled



$T_{\phi 1}$ set for MPPT
 $T_{\phi 2}$ set by ZCD

Trade off in "K. Chew et al., ISSCC 2013"

MISIMO Event Driven Controller

MISIMO Triggers

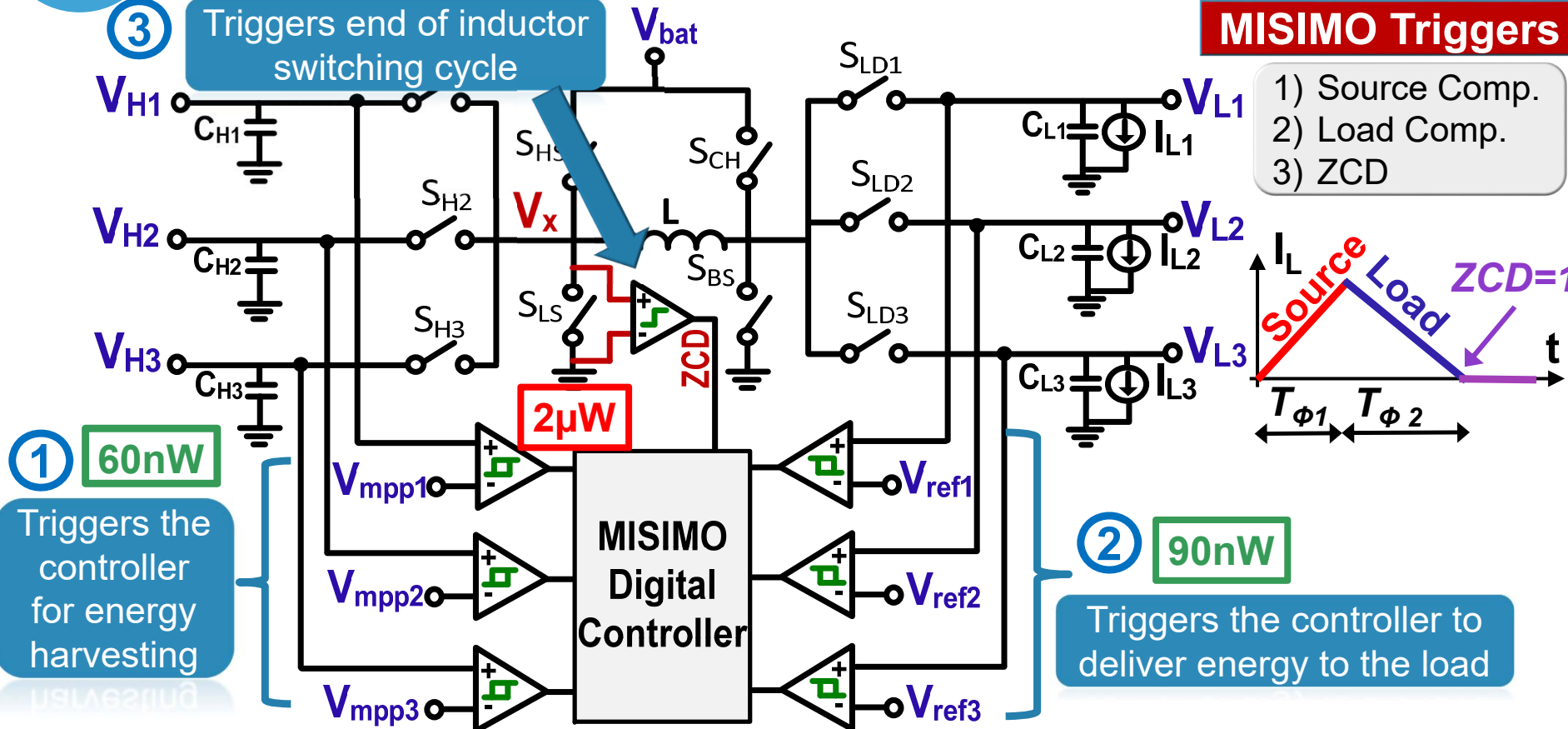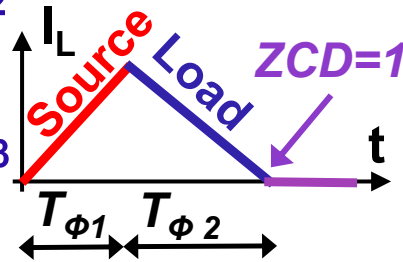- 1) Source Comp.
- 2) Load Comp.
- 3) ZCD



① **60nW**
Triggers the controller for energy harvesting

② **90nW**
Triggers the controller to deliver energy to the load




③ Triggers end of inductor switching cycle

1) Source Comp.
2) Load Comp.
3) ZCD




90nW

Triggers the controller to deliver energy to the load

MISIMO Measurement Results

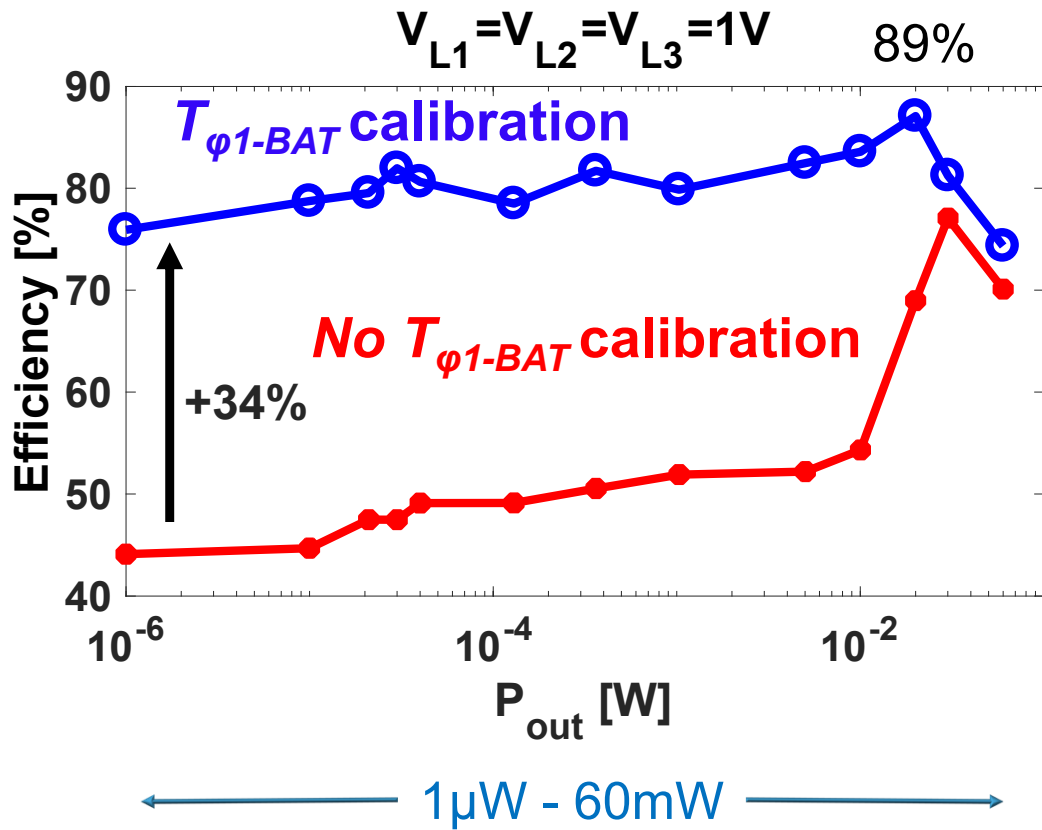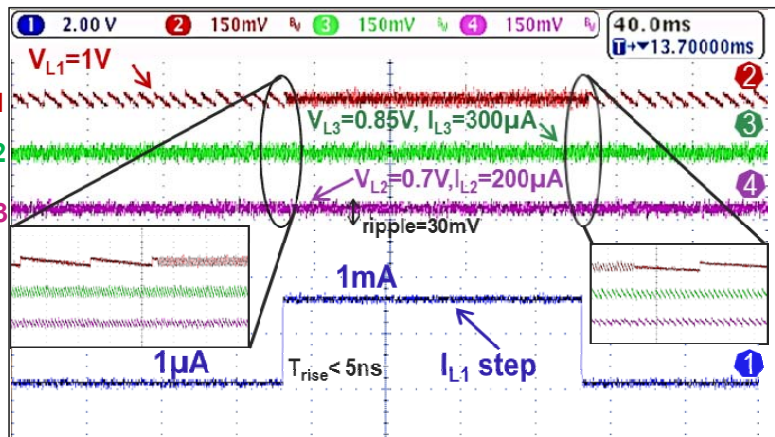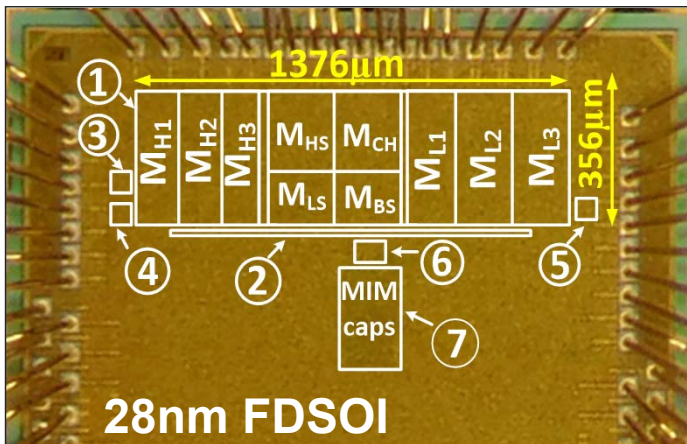

H-SIMO: Hybrid SIMO

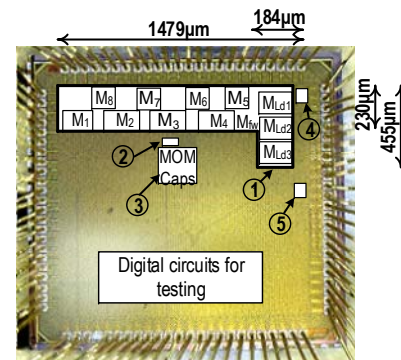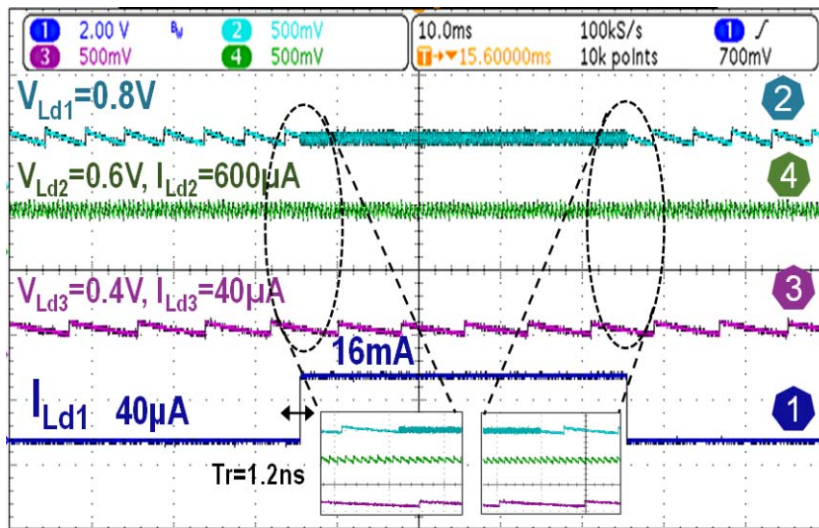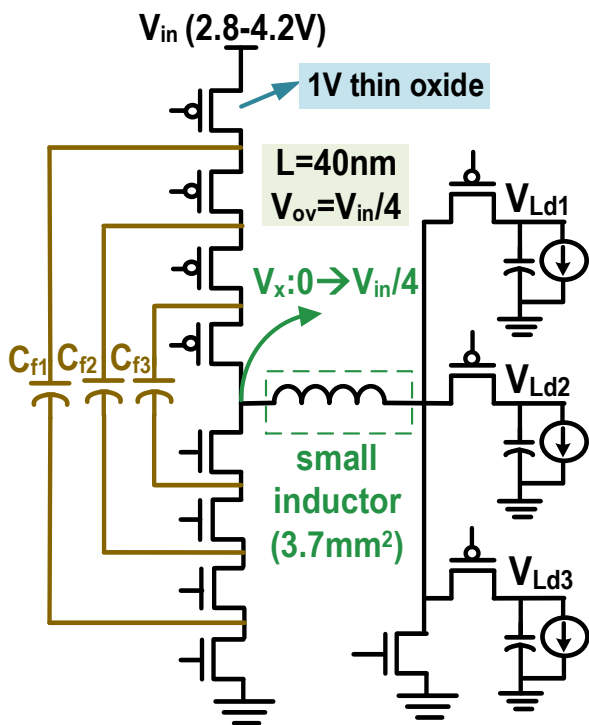

- Li-ion compatible in 28nm FDSOI
- Simultaneously regulates 3 loads w/ one inductor
- Peak efficiency = 91.4%
- 4,000x dynamic range w/ >70% efficiency



Harvesting energy from human perspiration via lactate biofuel cells



Watch "OFF"




Watch "ON"


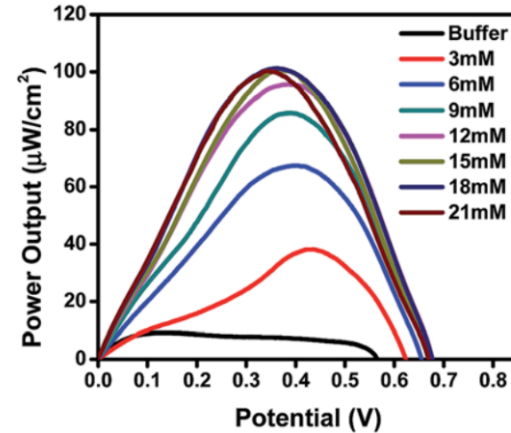
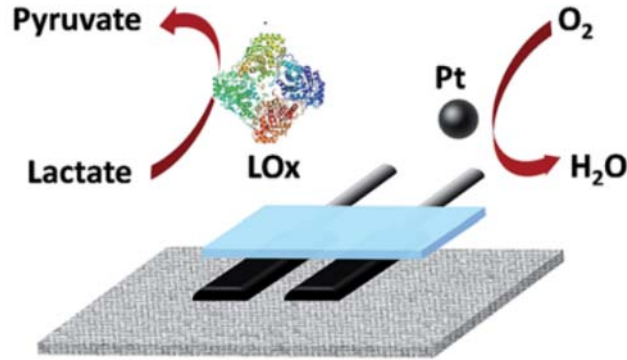


Increasing BFC power density

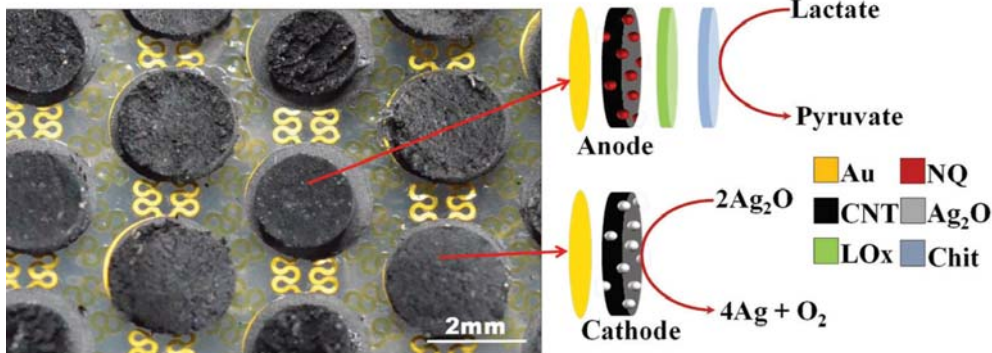
Islands-bridge structure enables high power density (**1mW/cm²**) while retaining stretchability





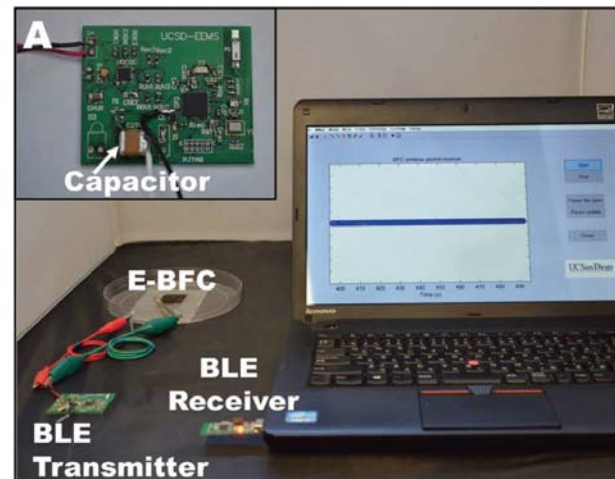
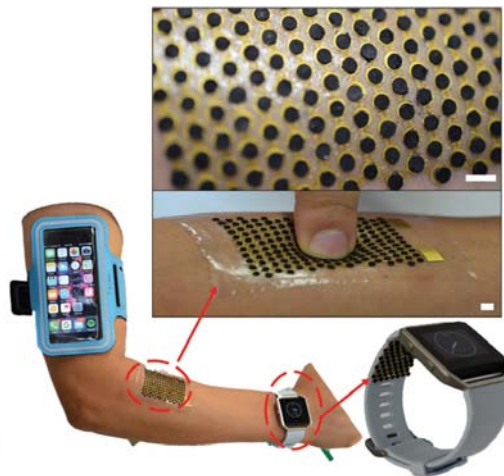
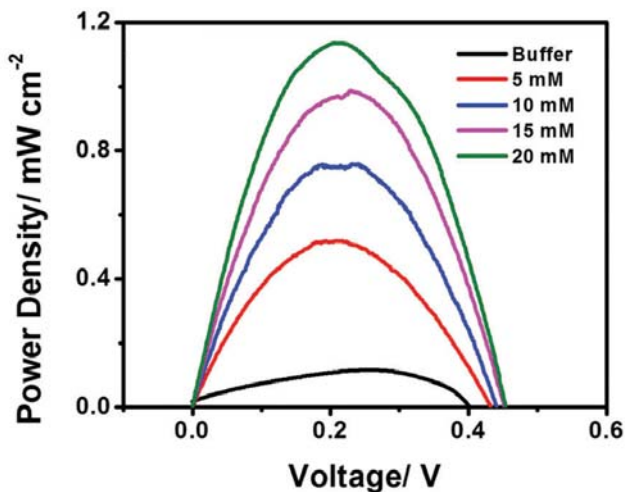
Sufficient power to operate a Bluetooth radio




Self-powered glucose sensing

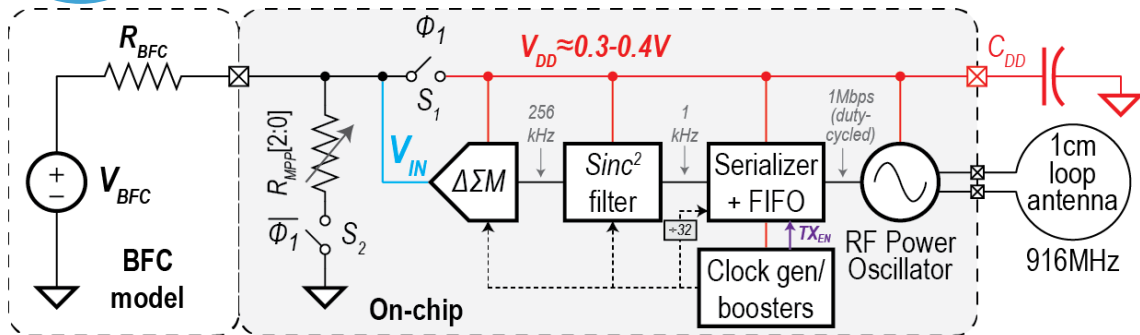

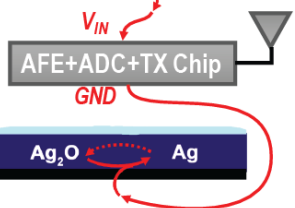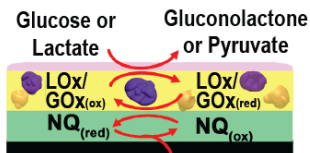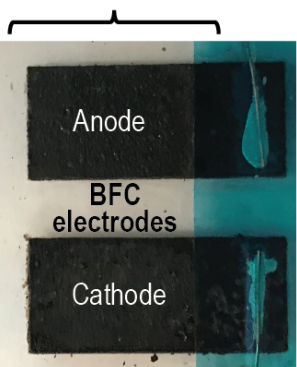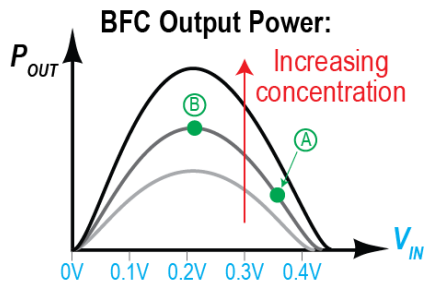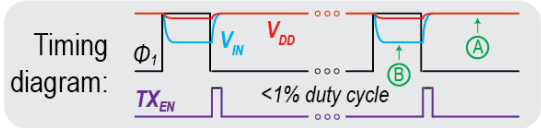
- No DC-DC converter
 - All circuits optimized to operate at 0.3V
- Full wireless capabilities
- $1\mu\text{W}$ average power



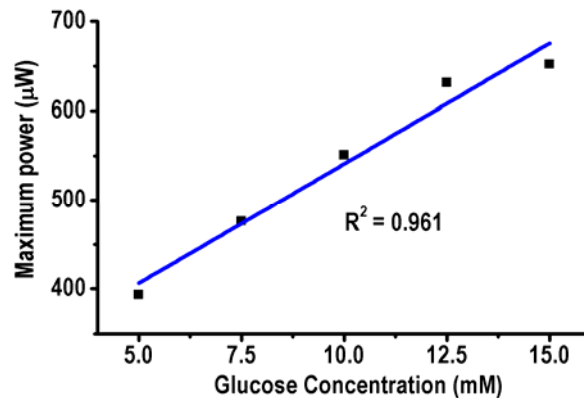- BFC Material Comp**
- GOx/LOx
 - BSA
 - Cl
 - Electrical collector
 - En
 - CNTs/NQ mediator nanocomposi
 - Ag₂O nanocomposite



Inductor-first conversion

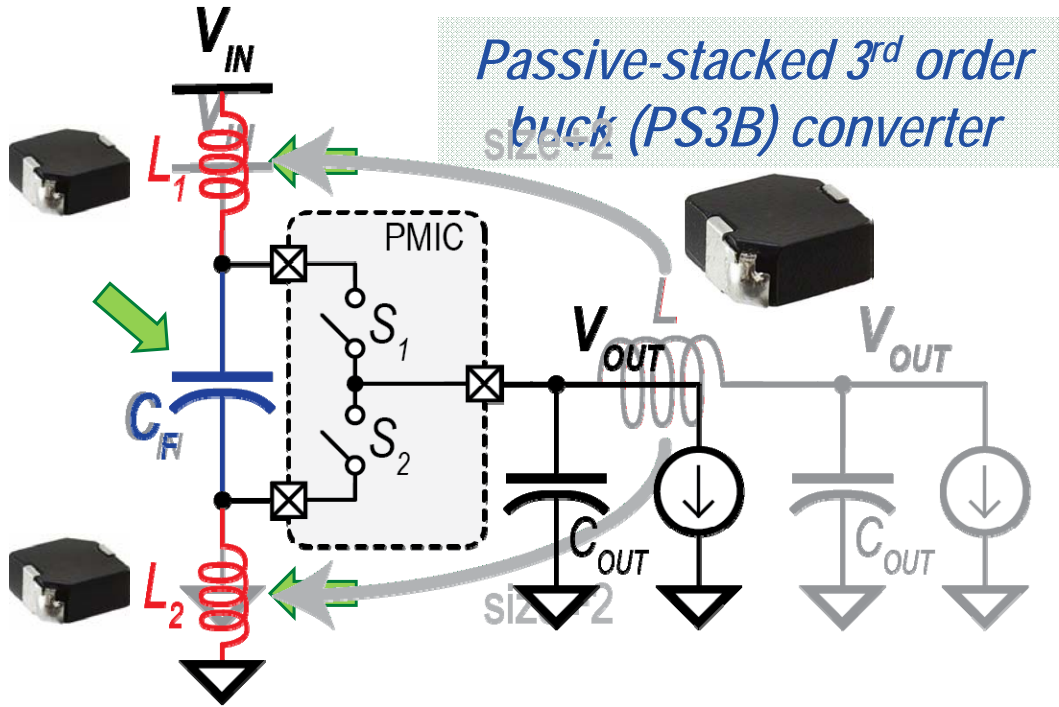

High Voltage
Low Current

Switches
(Small R_{ON})

Low Voltage
High Current

Small Inductor
(Large DCR)

V_{OUT}

Split into two half-sized inductors and stack at input


The input capacitor is now flying

All passives are stacked at input

Inductors are placed at the low-current side of the converter


PS3B Measurement Results

Top-side

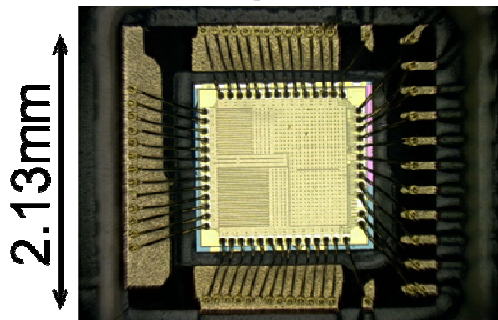


2.33mm

Bottom-side

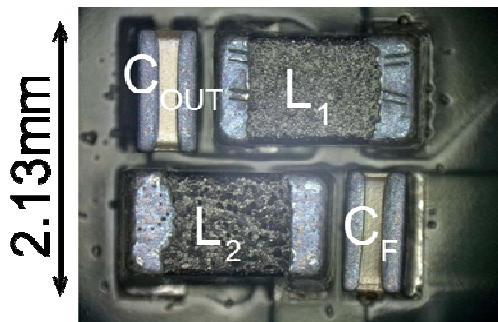

2.33mm

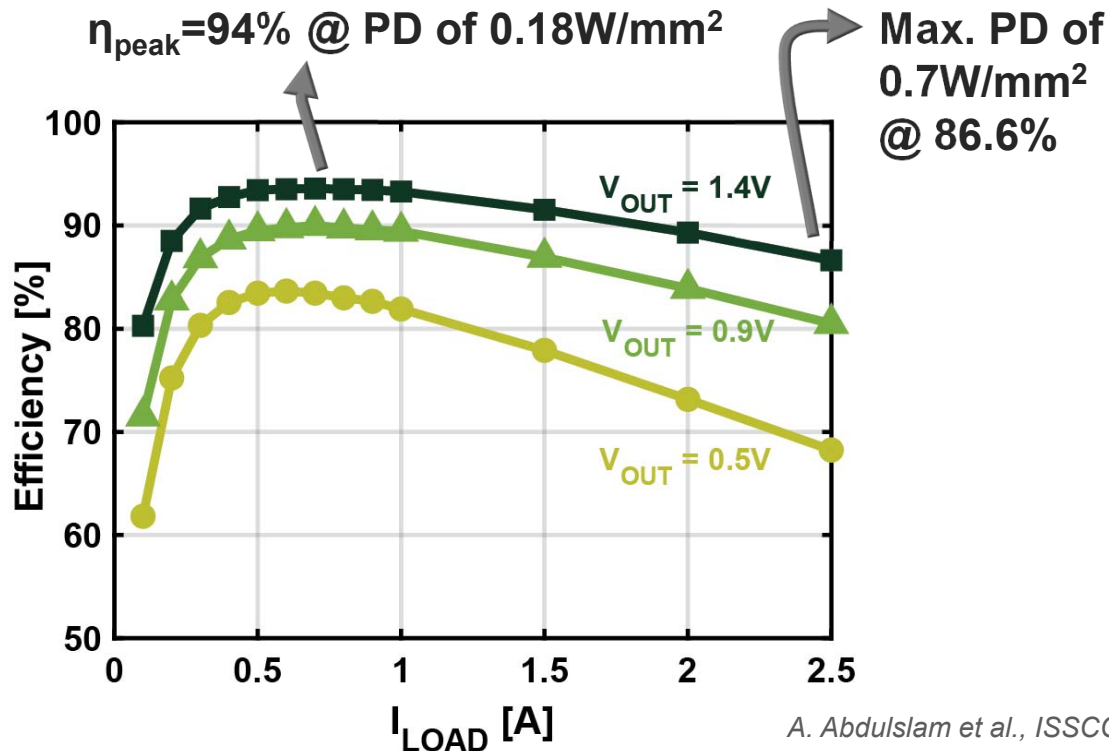


Benefits: reduced EMI and input noise, area-efficient stacked-passives, smaller inductors volume


- ❖ A symmetric modified multilevel ladder (SMML) converter:
 - Consists of two sides each with 2 capacitors and 6 switches.

❖ Features:



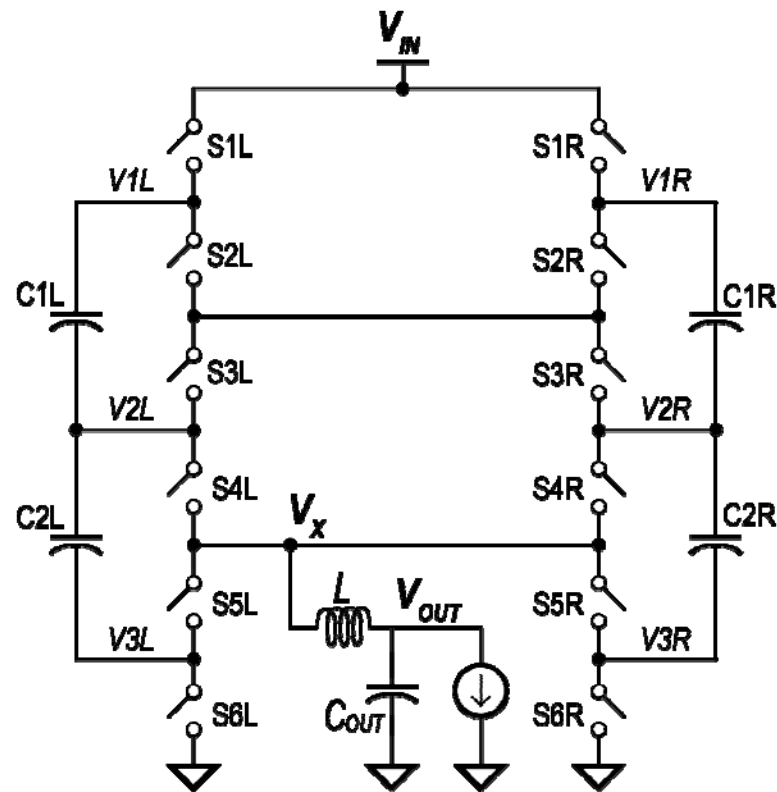
- ✓ **Decreased conduction losses** due to inherent phase interleaving.
- ✓ **Minimum blocking voltage** on all switches/capacitors.
- ✓ **No need for voltage balancing modules** flying capacitors are naturally stable.
- ✓ **All necessary supplies are generated internally** to power drivers and level shifters.




SMML Measurement Results

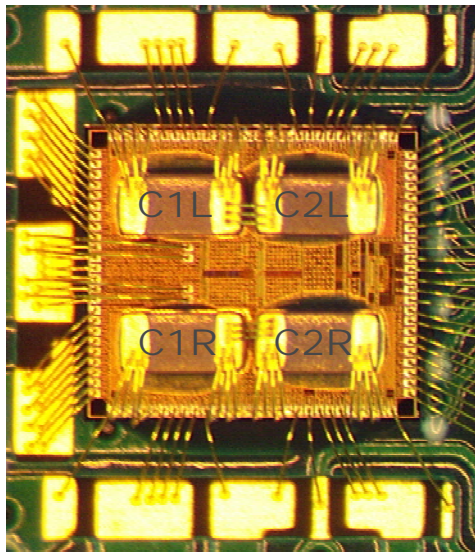

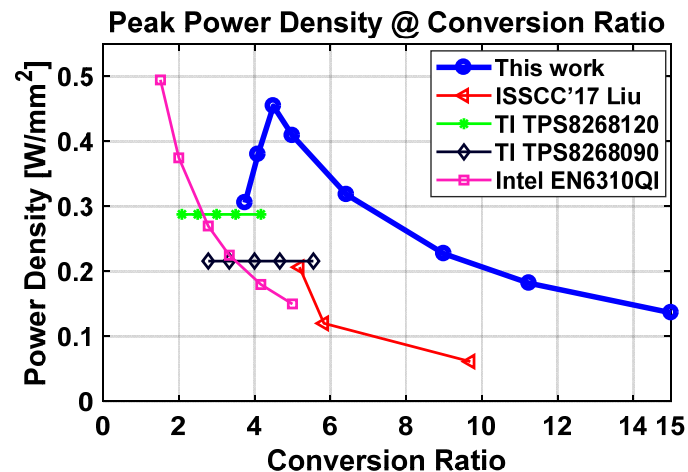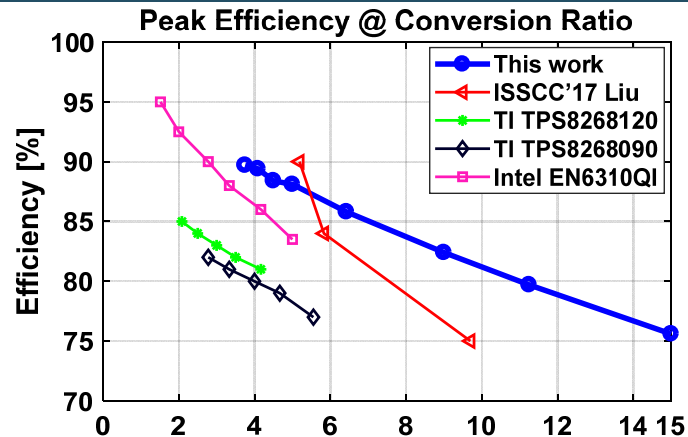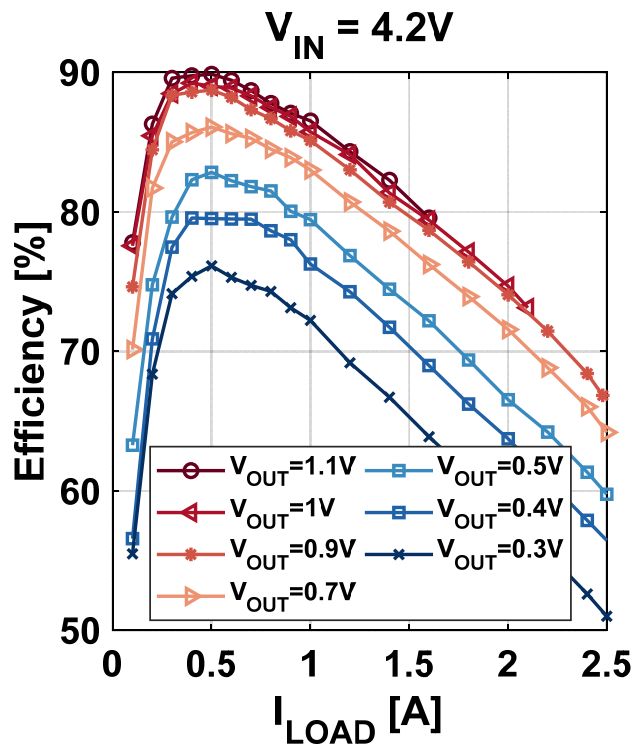The inductor and the output capacitor are mounted under the chip




CMOS Power Amplifier Voltage Challenge

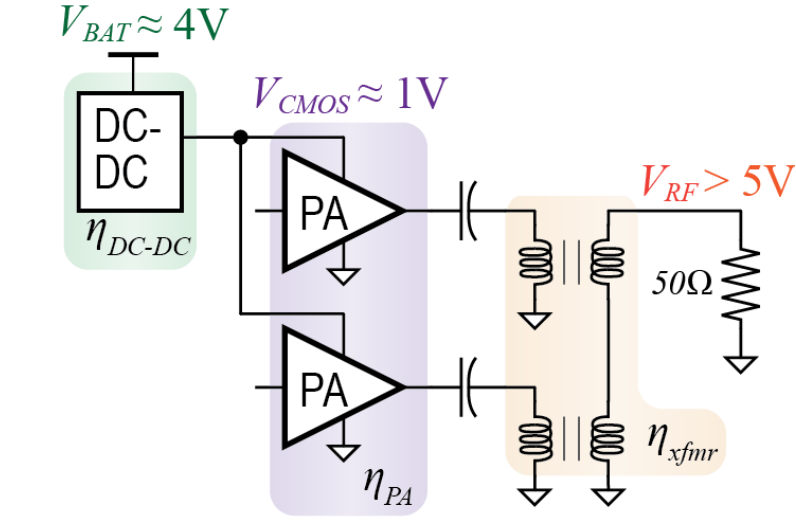

Idea: utilize many efficient $\sim 1V$ class-D PAs and combine power with transformers

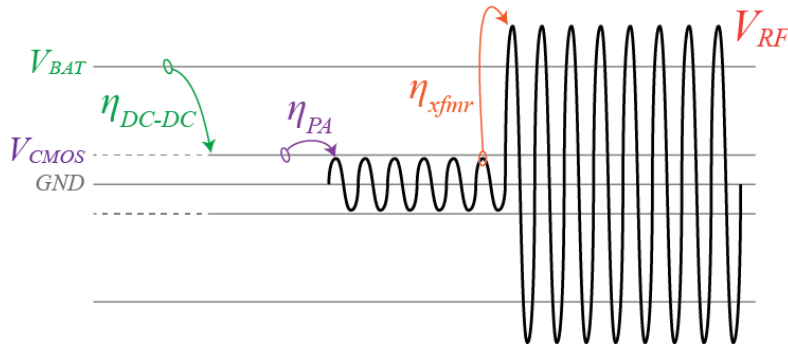Problem: three voltage conversion stages leads to cascaded losses:

$$\eta_{tot} = \eta_{DC-DC} \eta_{PA} \eta_{xfmr} < 30\%$$




Why do we go down, then back up in voltage?
There must be a better way!

Partial Solution: PA Stacking

Stack entire class-D PAs for current re-use:

~100% efficient *implicit* DC-DC conversion

(each PA sees only $V_{BAT}/2$)

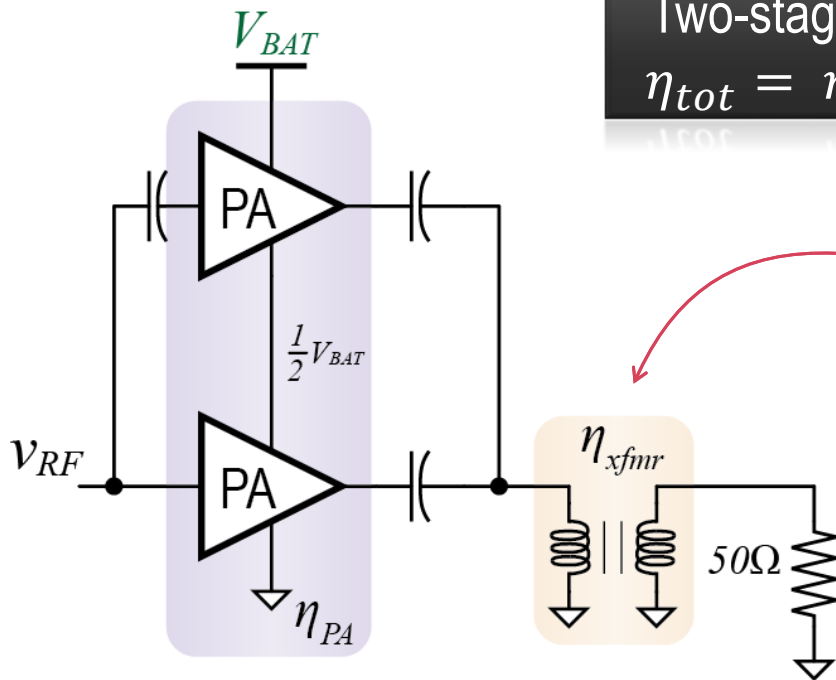


Two-stage cascade:

$$\eta_{tot} = \eta_{PA} \eta_{xfmr}$$

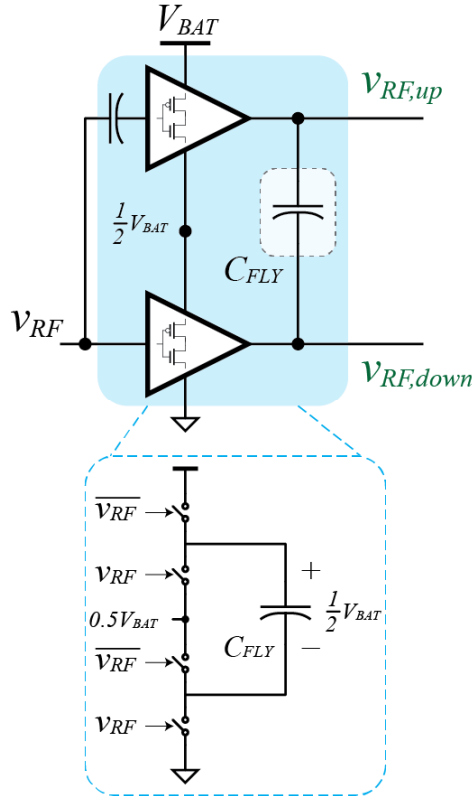
Problem: still require lossy transformer to achieve high output power in scaled CMOS

Solid-State RF Impedance Transformation

Idea: generate large RF voltages directly from a battery using $\sim 1V$ devices by stacking PAs, then flying subsequent PAs between the rails of the prior stages in a *House-of-Cards* Topology




Animation
not seen in print


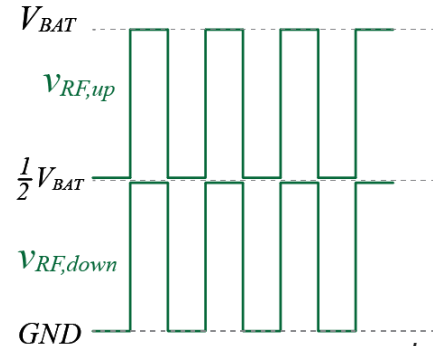


Solid-State RF Impedance Transformation

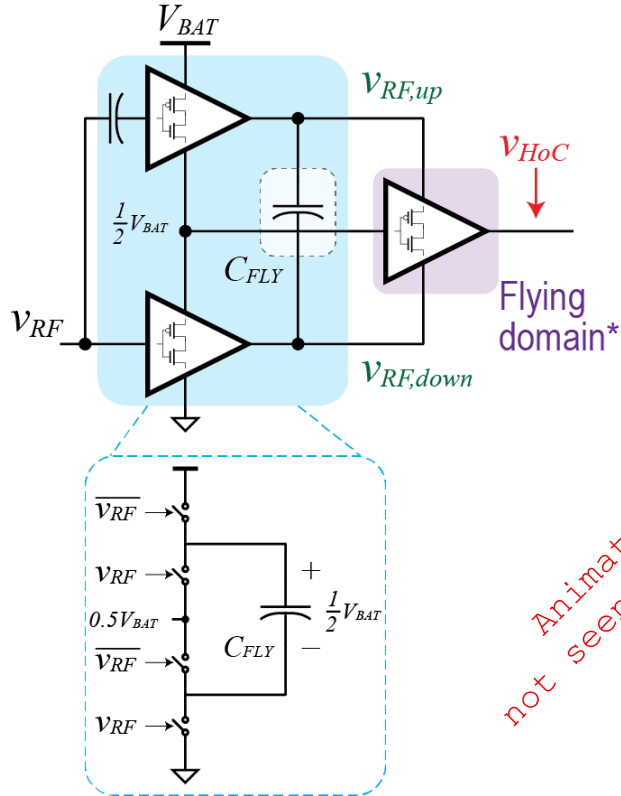Idea: generate large RF voltages directly from a battery using $\sim 1V$ devices by stacking PAs, then flying subsequent PAs between the rails of the prior stages in a *House-of-Cards* Topology






Animation
not seen in print

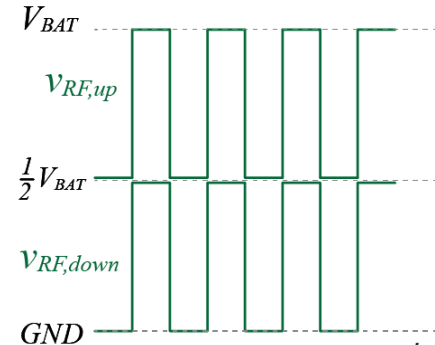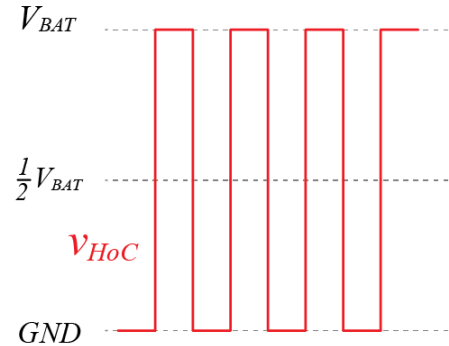


Solid-State RF Impedance Transformation

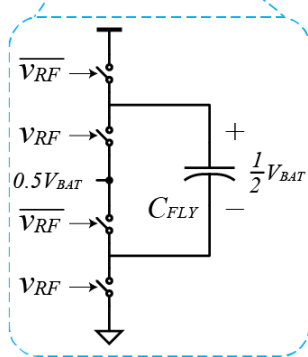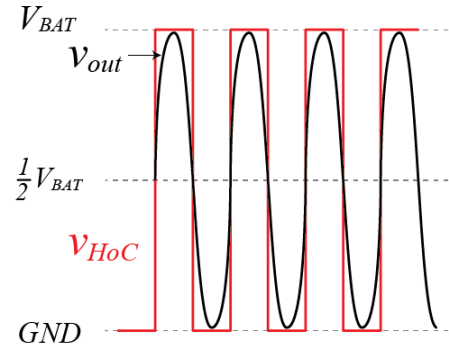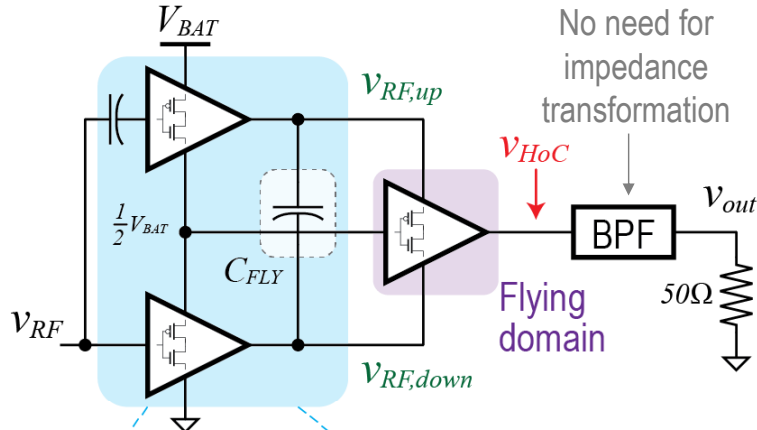Idea: generate large RF voltages directly from a battery using $\sim 1V$ devices by stacking PAs, then flying subsequent PAs between the rails of the prior stages in a *House-of-Cards* Topology




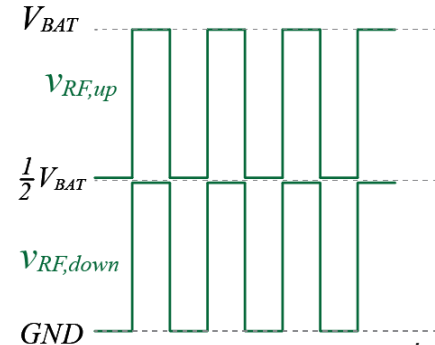High power RF waveform synthesized directly from V_{BAT} using low-voltage transistors




*For more information, see Salem et al., ISSCC'16


House-of-Cards (HoC) Schematic

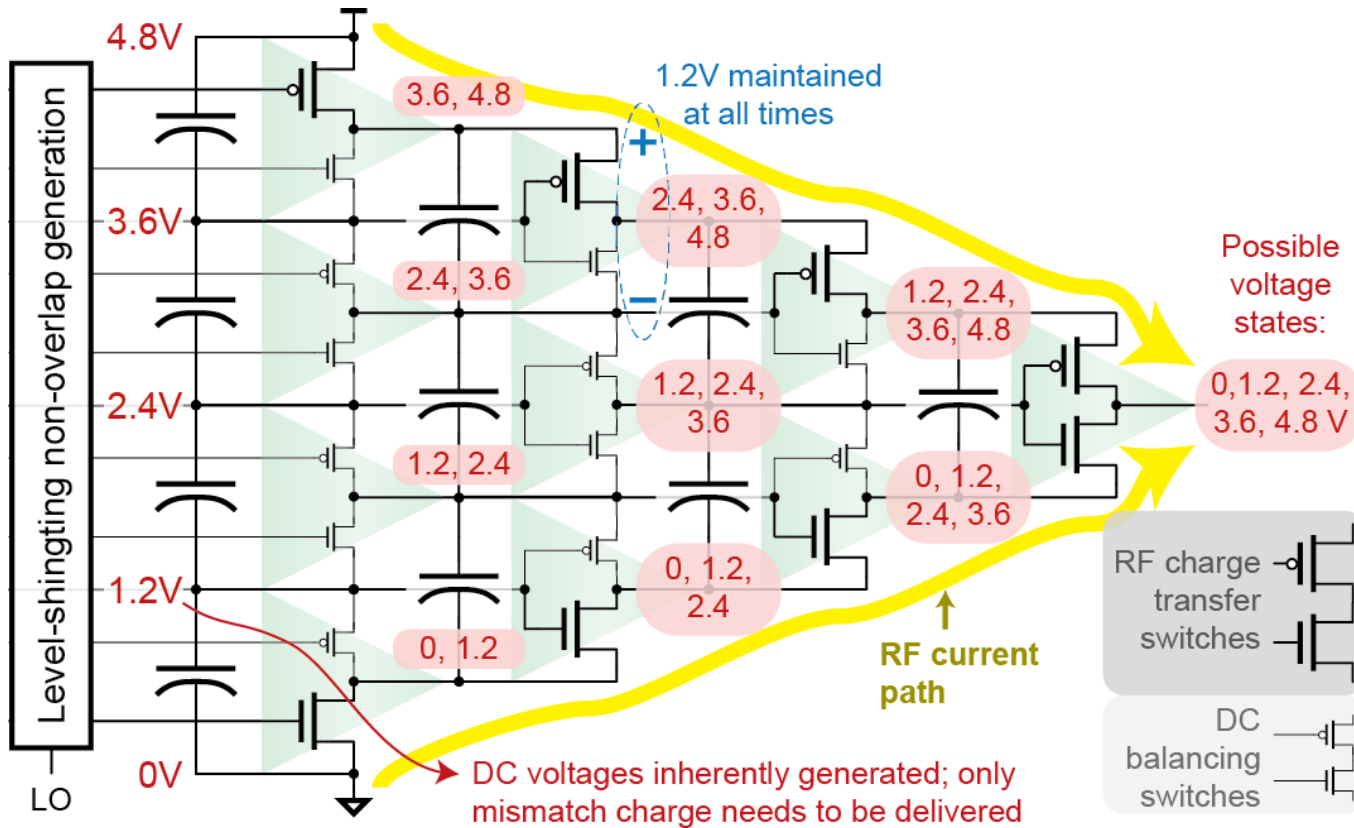

Measurement results: PAE

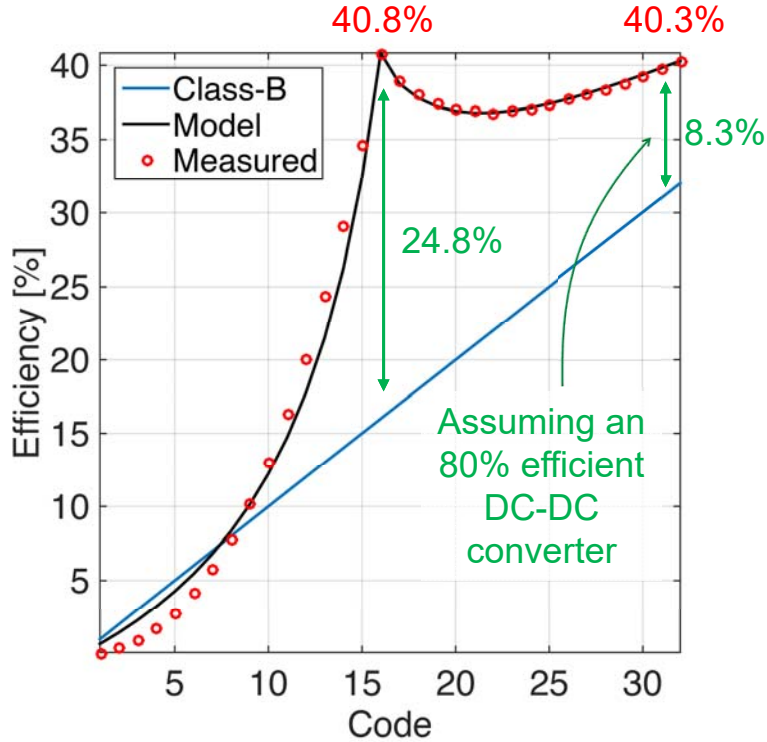


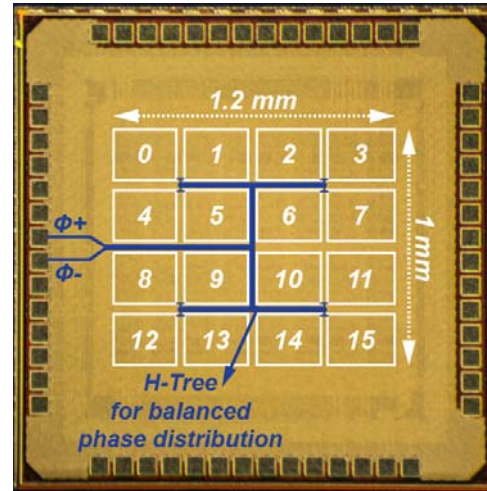65nm LP
1.2V transistors
Direct 4.8V Li-ion battery connection



>40% battery-to-RF power-added efficiency at both peak power (23dBm) and at 6dB backoff



A nW Wake-up Receiver

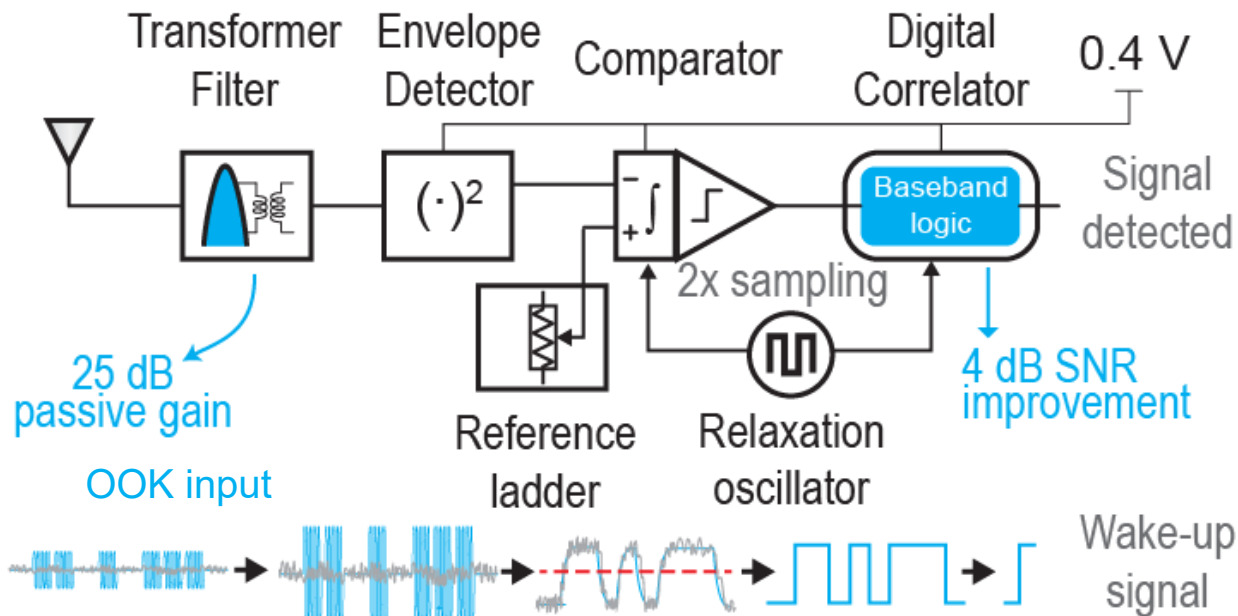

High R_{in} ED supports high passive gain front-end w/ high-Q filtering at low power

WuRX Measurement Results

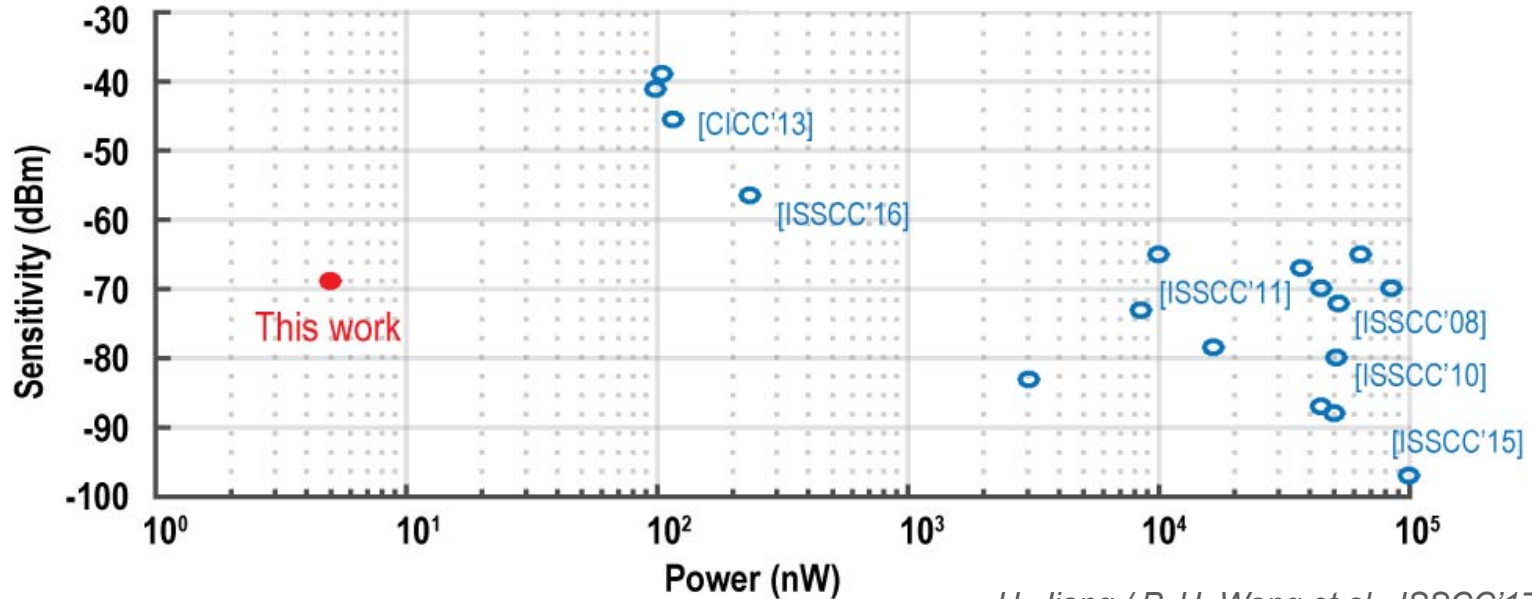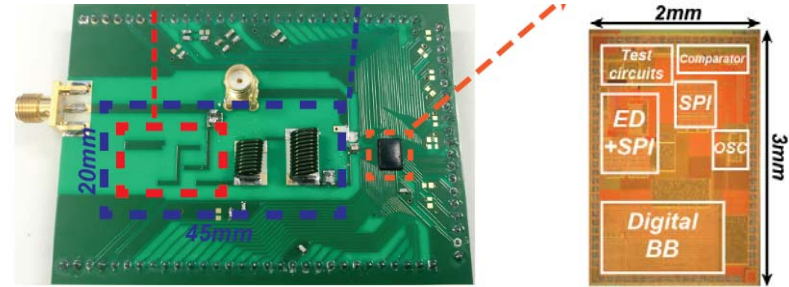- Power consumption: 4.5nW
- Sensitivity: -69dBm
- Wake-up latency: 53ms



Challenge: standards compliance

Most standards use complex modulation at high data rates
→ difficult to build an ultra-low-power RX w/ good sensitivity




Back-channel communication

Hack a standard-compliant signal to look like a simpler, lower bandwidth modulation

N. E. Roberts et al., ISSCC'16


Example:

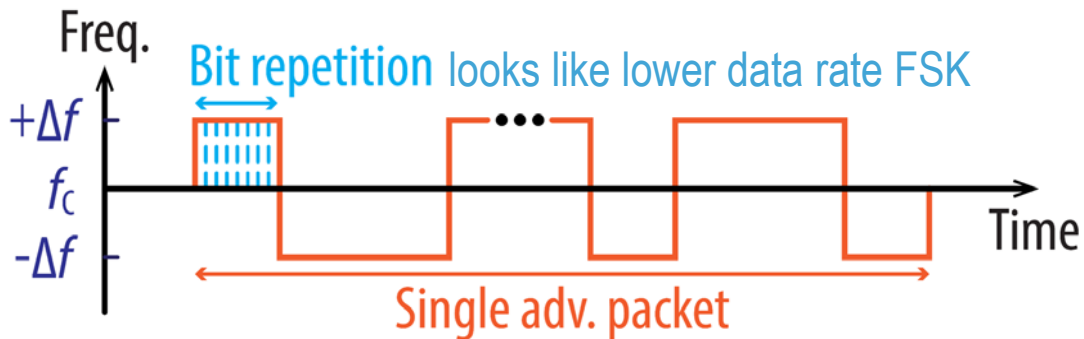

M. R. Abdelhamid et al., CICC'18



An Interference-Robust BLE-Compliant WuRX

BLE advertising event structure

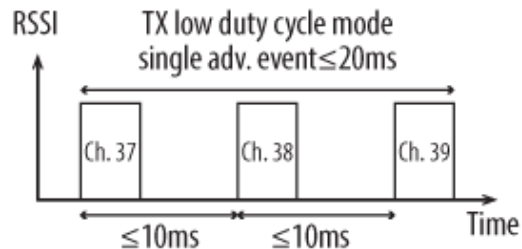

BLE advertising channels and wireless co-existence @ 2.4GHz ISM band

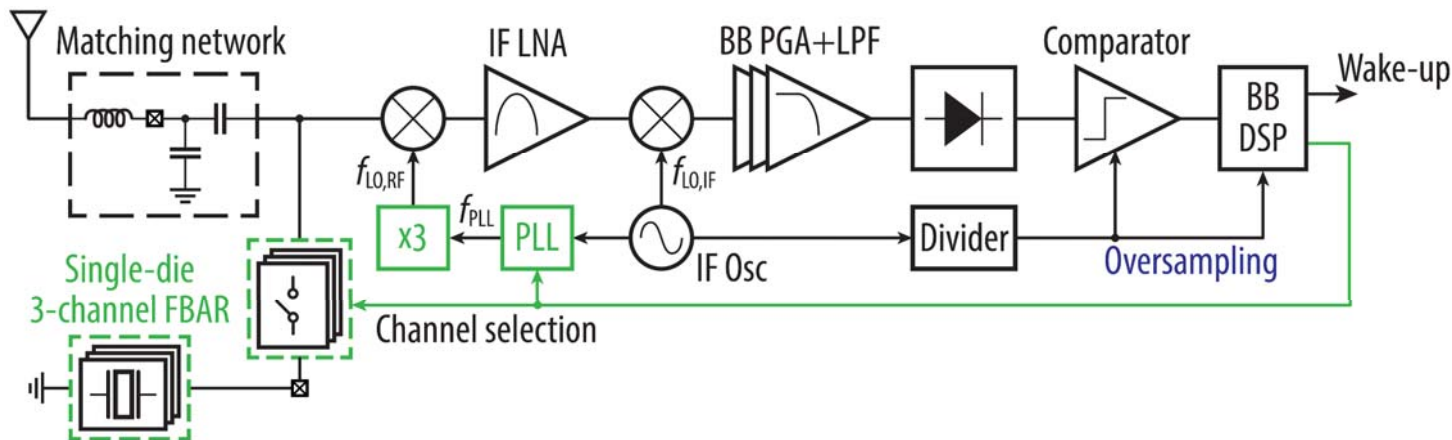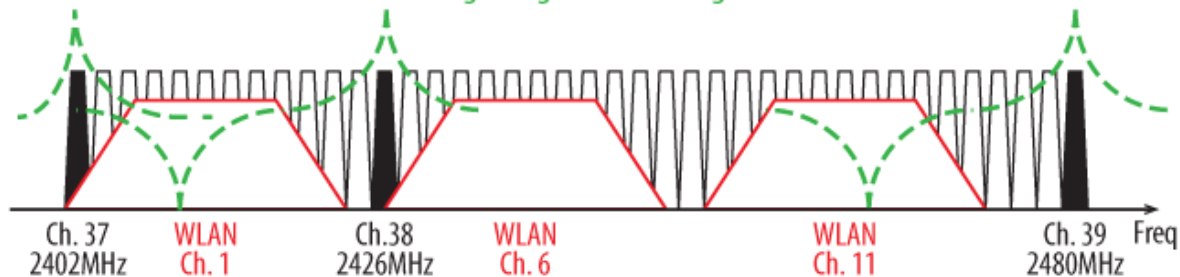
Direct channel-filtering using 0.25mm^2 single-die 3-channel FBAR






Frequency-hopping between advertising channels enables interference-resilient detection

detection

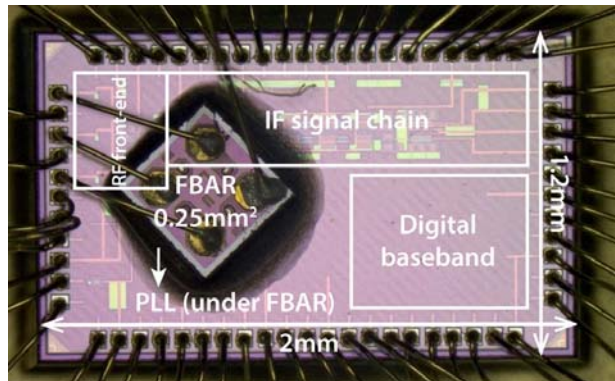An Interference-Robust BLE-Compliant WuRX



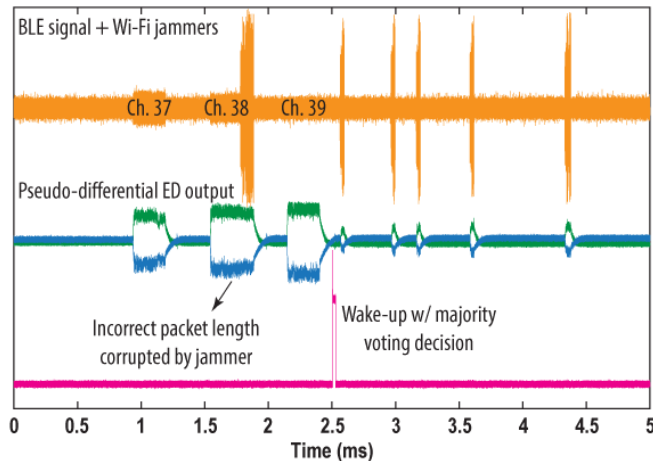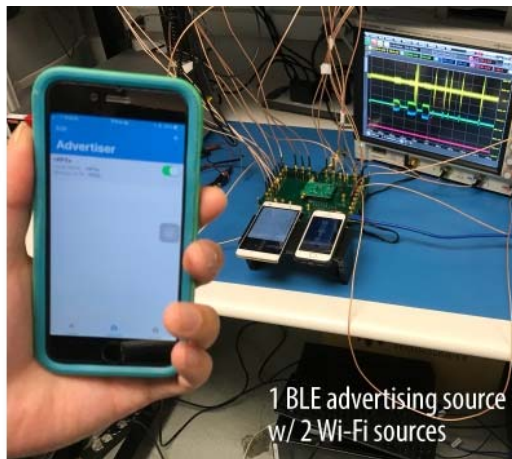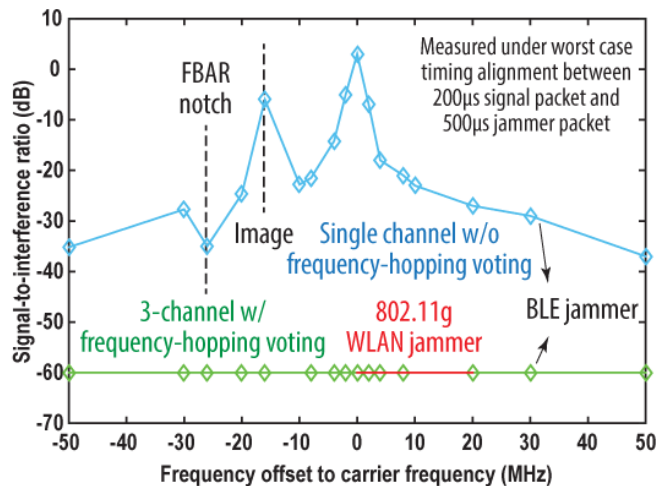- ❑ **Sensitivity:** -85dBm @ 220 μ W
 - ❑ 27.5dB better than prior-art
- ❑ **Latency:** 200 μ s-to-1.47ms
- ❑ **SIR:** at least -60dB SIR (limited by measurement setup)



- Next generation IoT devices require:
 - New sensors and sensing techniques
 - Small form factors
 - Long/infinite battery life → often limited by radios
- Meet these needs through:

Application Engineering

- New communication paradigms
- New sensor development

Architectural Innovations


- New sensor transduction/digitization techniques
- New power conversion circuit topologies

New Circuit Techniques

- Topologically-defined “digitally-replaced analog”
- Deep subthreshold DTMOS



Exciting new
IoT
applications!

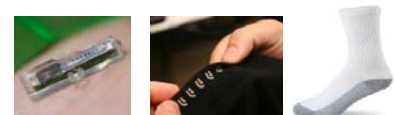



Acknowledgements



FOUNDATION



UC San Diego

JACOBS SCHOOL OF ENGINEERING
Center for Wireless Communications

